

unit - IV


Transistor Biasing and stabilization.

Operating point:


Operating point: A transistor must be properly biased with a dc voltage in order to operate as an amplifier. A dc operating point must be set so that signal variations at the input terminal are amplified and accurately reproduced at the output terminals. The dc operating point is often referred to as the Q-point (quiescent point) (if signal will be equal to

zero i.e AC signal). It apply only DC signal as


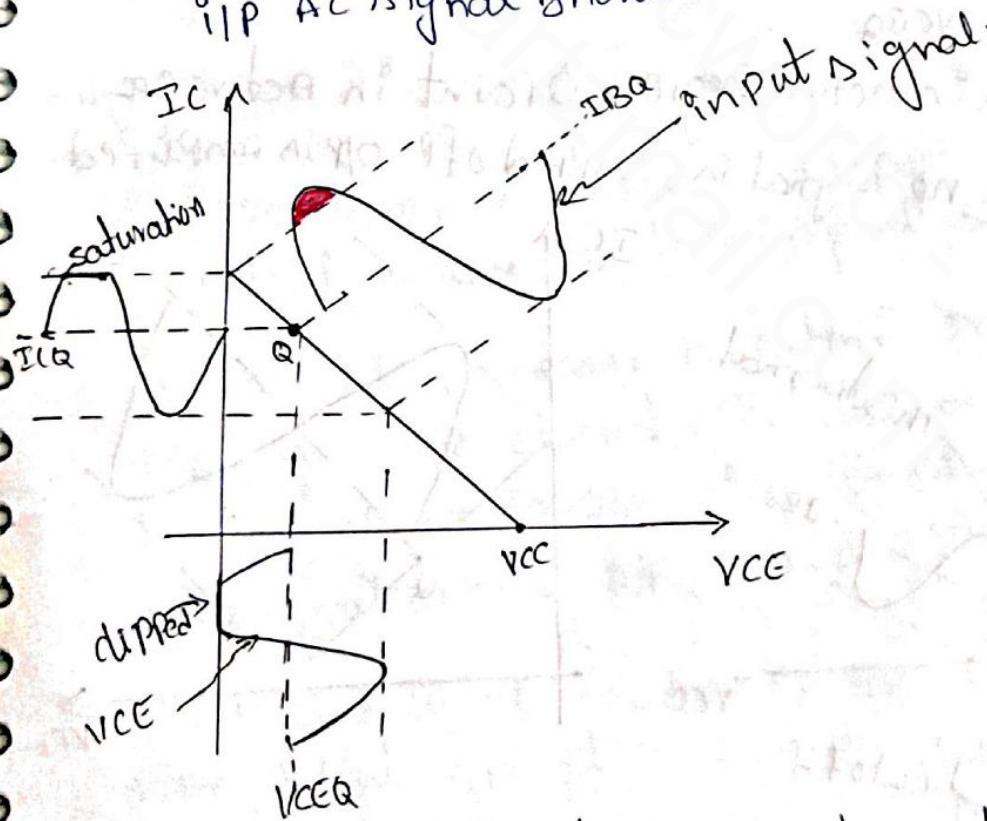
zero i.e AC signal).
 For finding opoint apply only DC signal as
 if AC signal should be equal to zero.
 E. Signal.



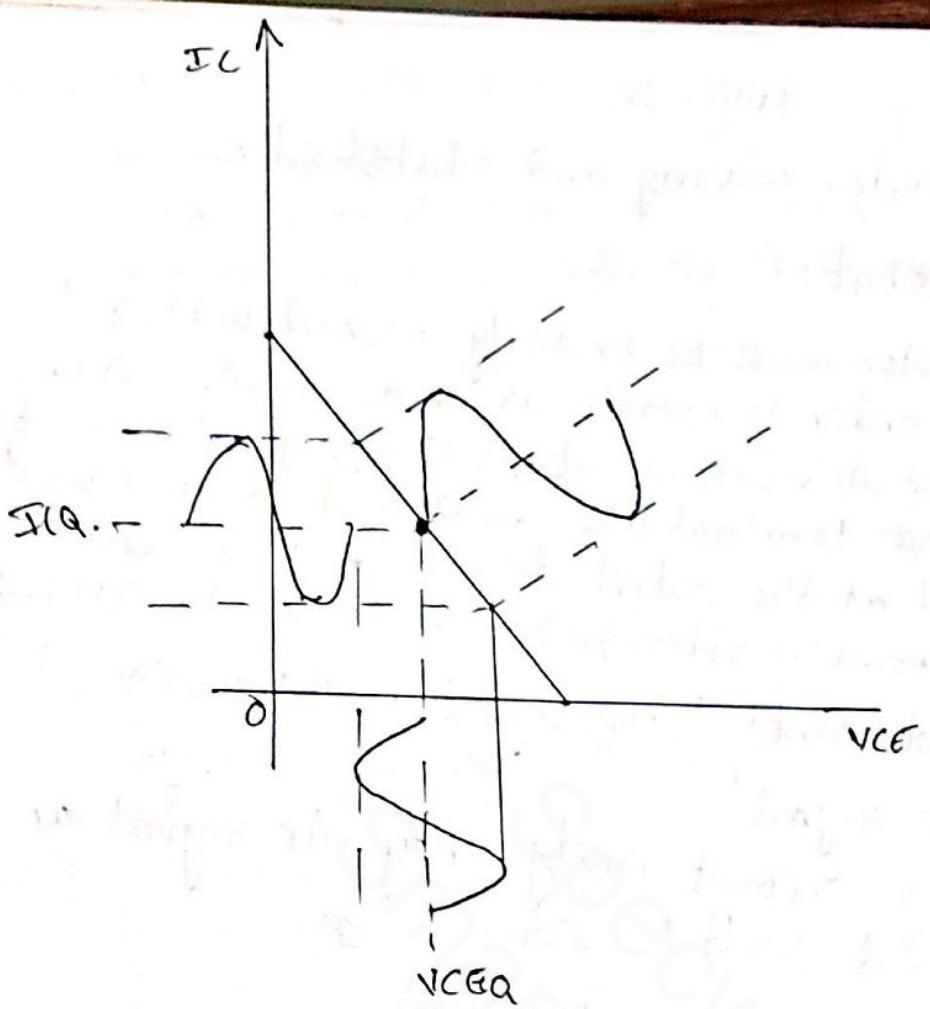
V_{CEQ} transistor is driven into saturation because the Q-point is too close to saturation for the given input signal.



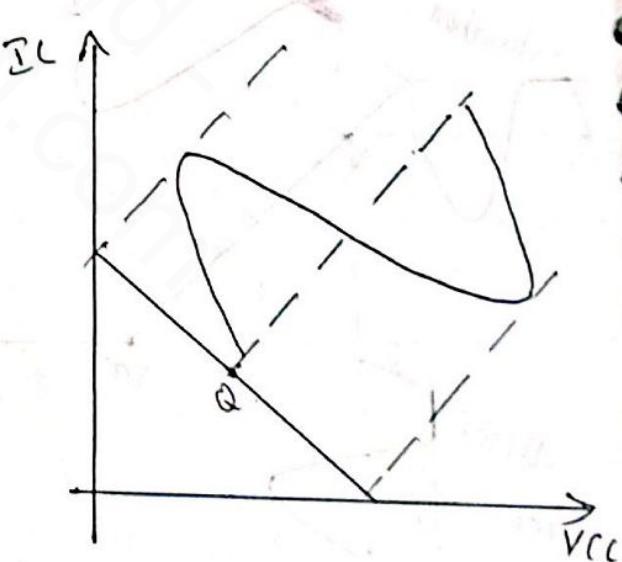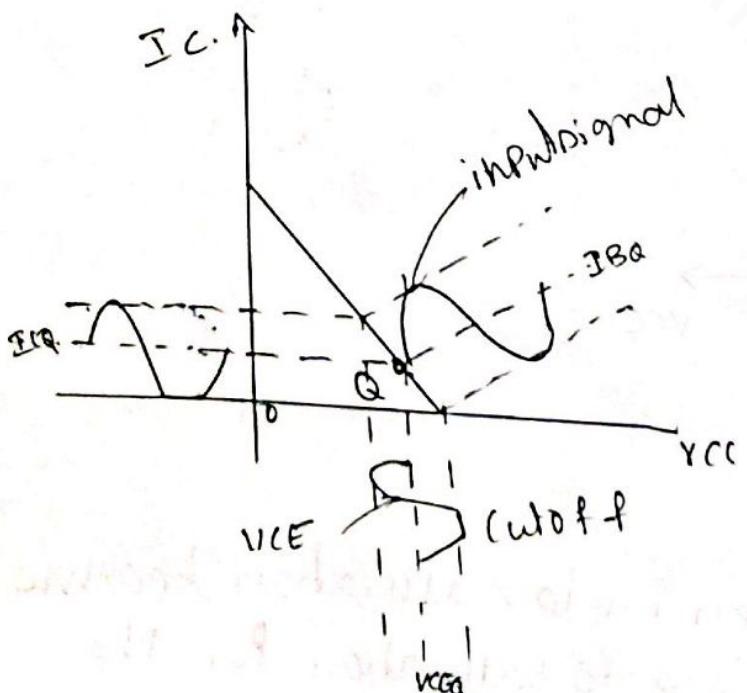Transistor is in active region. Q point is in active region center then no signal is clipped off opp is amplified.



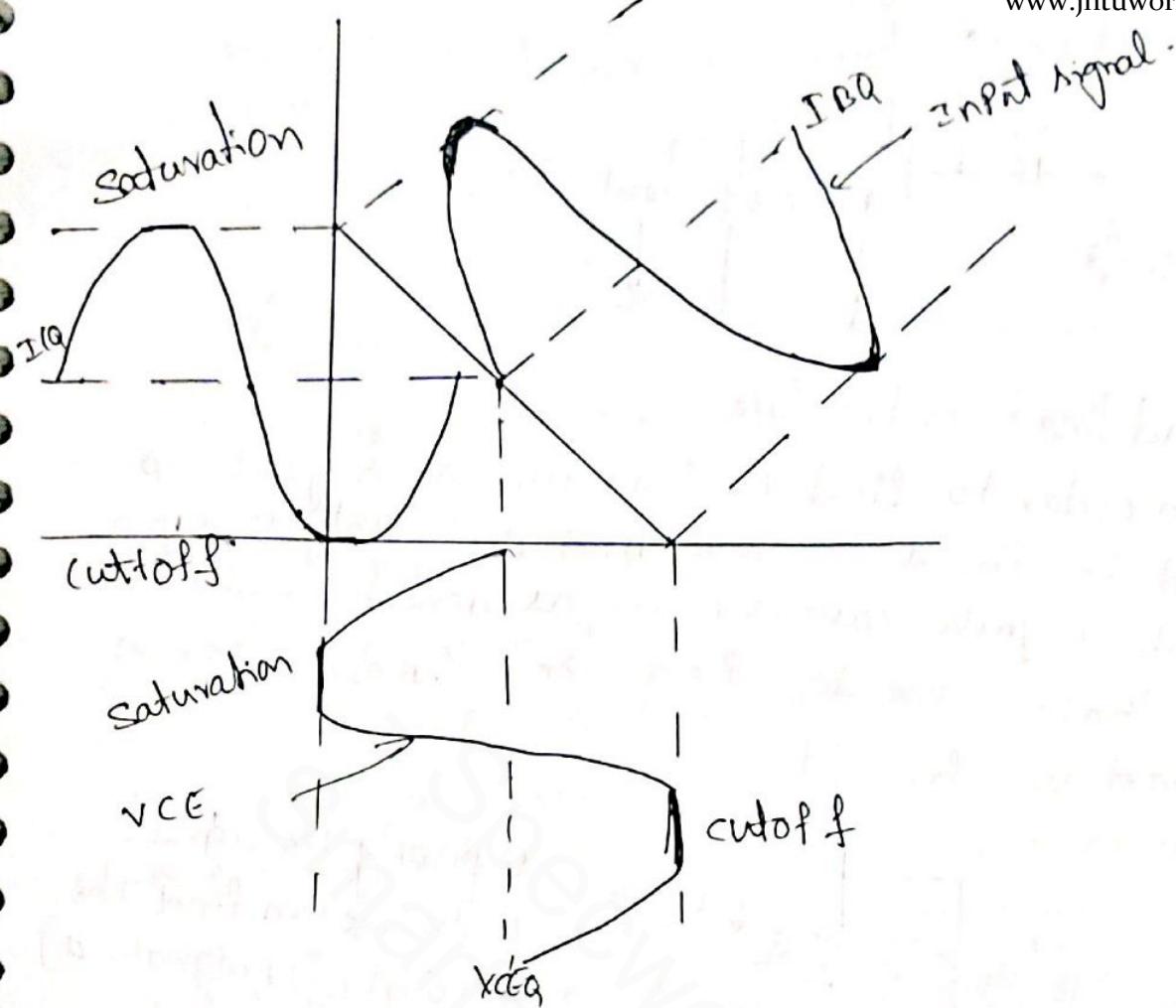Transistor is driven into cutoff because the Q point is too close to cutoff for the given input signal



Transistor is driven into both saturation & cutoff because the input signal is too large.


If Q point is nearer to cutoff or saturation then the signals are clipped off, from above figure. If the i_p signals are larger than beyond the cutoff or saturation also signals at the o/p will be clipped off

If Q point is at center as i_p AC signal is small then output signal is replica of i_p signal.

To maintain Q point at center are two reasons

1. To act as an amplifier

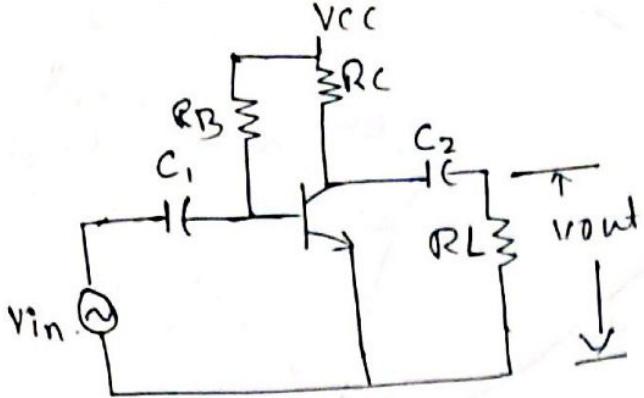2. If Q carries o/p signal is not replica of i_p signal.




DC load line: DC load line

In order to find DC load line, AC signal \hat{V}_{IP} should be equal to zero. And apply only DC signal for DC signals capacitor act as opened since $X_C = \frac{1}{2\pi f} C$ for DC $f=0$ $X_C = \infty$

$$X_C = \frac{1}{2\pi f} C \quad \text{for DC} \quad f=0 \quad X_C = \infty$$

So redraw the ckt.

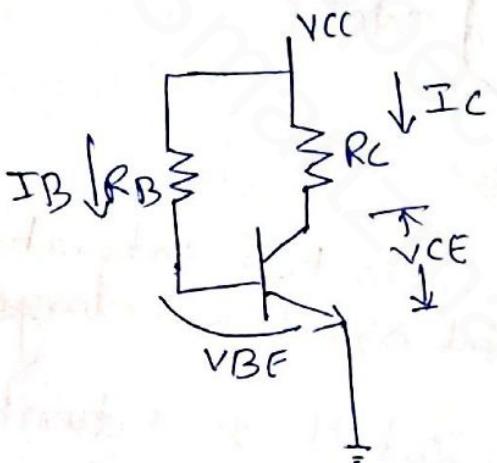

By apply DC signal only we can find the Q point ($\hat{V}_{IP} = 0$)

For load line analysis we have to do the


- actual characteristics of CE characteristics
- draw a straight line is called load line by applying Kirchhoff's law to the ckt to find where it touches x-axis w/ y-axis.

To find a point:

- combine both actual characteristics of CE w/ load line Kirchhoff's law. (Touching x-axis w/ y-axis find out)

↳ Find mid point of xaxis w/ yaxis is Q Point.

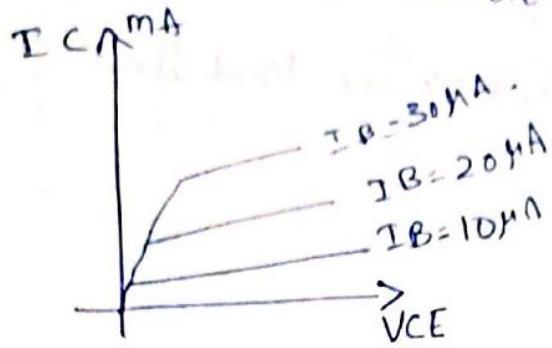1. Draw the actual characteristics of CE characteristics.



2. Apply Kirchhoff Law to the ckt to find I_{C} related to V_{CE} w/ I_{C} .

$$\text{V}_{\text{CC}} = \text{I}_{\text{C}} \cdot \text{R}_C + \text{V}_{\text{CE}}$$

x-axis touches when $\text{I}_{\text{C}} = 0$

$$\text{V}_{\text{CC}} = \text{V}_{\text{CE}} \Rightarrow \boxed{\text{V}_{\text{CE}} = \text{V}_{\text{CC}}}$$

I_{Cmin} we get minimum collector current when the subtraction term $\frac{\text{V}_{\text{CE}}}{\text{R}_C}$ in eqn (a) is maximum.

$\text{V}_{\text{CC}} = \text{I}_{\text{C}} \cdot \text{R}_C + \text{V}_{\text{CE}} \Rightarrow \text{I}_{\text{C}} = \frac{\text{V}_{\text{CC}} - \text{V}_{\text{CE}}}{\text{R}_C} = \frac{\text{V}_{\text{CC}}}{\text{R}_C} - \frac{\text{V}_{\text{CE}}}{\text{R}_C} \quad @$
that is what we have applied supply that will be the drop.

$$\text{V}_{\text{CE}} (\text{drop}) = \text{V}_{\text{CC}} (\text{Supply})$$

$$\text{I}_{\text{C}} = \frac{\text{V}_{\text{CC}}}{\text{R}_C} - \frac{\text{V}_{\text{CE}}}{\text{R}_C} \Rightarrow \text{I}_{\text{Cmin}} = \frac{\text{V}_{\text{CC}}}{\text{R}_C} - \frac{\text{V}_{\text{CC}}}{\text{R}_C} = 0$$

$$\text{x-axis point} = (\text{V}_{\text{CC}}, 0)$$

y-axis touches when $\text{V}_{\text{CE}} = 0$

$$\text{V}_{\text{CC}} = \text{I}_{\text{C}} \cdot \text{R}_C + \text{V}_{\text{CE}}$$

$$\text{V}_{\text{CC}} = \text{I}_{\text{C}} \cdot \text{R}_C + 0$$

$$\boxed{\text{I}_{\text{C}} = \frac{\text{V}_{\text{CC}}}{\text{R}_C}}$$

I_{Cmax} we get maximum collector current if subtraction term the $\frac{\text{V}_{\text{CE}}}{\text{R}_C}$ is minimum. $@$

$$\text{I}_{\text{C}} = \frac{\text{V}_{\text{CC}}}{\text{R}_C} - \frac{\text{V}_{\text{CE}}}{\text{R}_C}$$

It implies we get maximum collector current I_{Cmax} when $\text{V}_{\text{CE}} = 0$ i.e. where the load line if touches the y-axis.

$$\text{I}_{\text{Cmax}} = \frac{\text{V}_{\text{CC}}}{\text{R}_C} - 0$$


$$\boxed{\text{I}_{\text{Cmax}} = \frac{\text{V}_{\text{CC}}}{\text{R}_C}}$$

y-axis =

www.inteworldupdates.org

y axis point ($V_{CE} = 0, I_C = V_{CC}/R_C$) ($0, \frac{V_{CC}}{R_C}$)

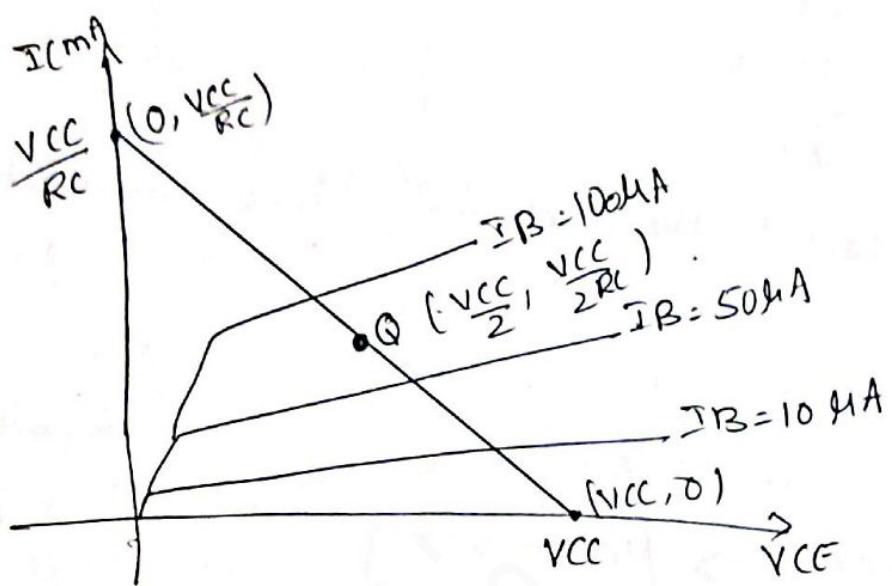3. combine actual CE characteristics w/ load line



4. find the mid point for x axis term w/ y axis term.

$$Q = \left(\frac{0 + V_{CC}}{2}, \frac{\frac{V_{CC}}{R_C} + 0}{2} \right) \quad \therefore \quad V_{CE} = 0 + V_{CE} = V_{CC}$$

$$I_{C\max} = \frac{V_{CC}}{R_C} + I_{C\min} = 0$$

Q Point is Mid Point $Q = \left(\frac{V_{CC}}{2}, \frac{V_{CC}}{2R_C} \right)$


AC load line : Ac load line.

Q Point is located at the center of load line.
Q Point is found at the zero input AC signal condition of the circuit.

To draw the AC load line we have to apply both AC signals w/ DC signals. So that AC load line should also pass through the operating point Q.

Since we are applying AC signal supply the capacitors act as short circuit.

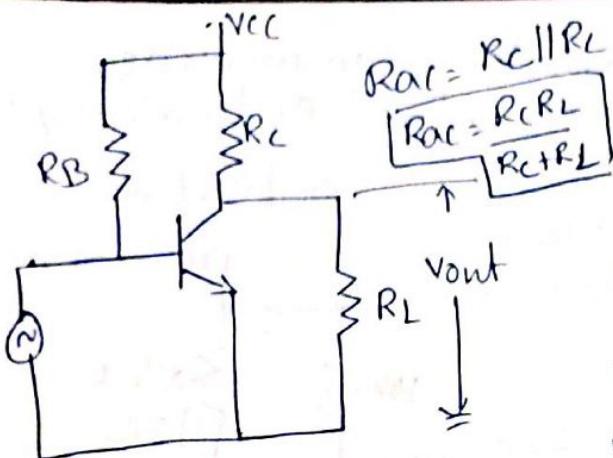For AC load line the resistance at output R_{AC} is combination of R_C & R_L from fig.



To draw the ac load line two end points & maximum V_{CE} w.r.t maximum I_C when the signal is applied are measured.

maximum $V_{CE} = V_{CEQ} + I_{CQ} \cdot R_{AC}$
on the V_{CE} axis

maximum $I_C = I_{CQ} + \frac{V_{CEQ}}{R_{AC}}$

which locates the point on the I_C axis.

V_{CE} : For AC load line both AC w. DC.

$$V_{CEDC} = V_{CEQ} = \frac{V_{CC}}{2}$$

$$V_{CE} = V_{CEDC} + V_{CEAC}$$

$$V_{CE} = \left(\frac{V_{CC}}{2} + \frac{V_{CC} \cdot R_{AC}}{2R_C} \right)$$

$$V_{CEAC} = \frac{I_{CQ} \cdot R_{AC}}{R_C}$$

$$V_{CEAC} = I_{CQ} \cdot R_{AC}$$

$$I_{LQ} = \frac{V_{CC}}{2R_C}$$

$$V_{CEAC} = \frac{V_{CC}}{2R_C} \cdot R_{AC}$$

$$I_C = I_{CDDC} + I_{CAC}$$

$$= I_{LQ} + I_{CAC}$$

$$I_{CDC} = I_{LQ} = \frac{V_{CC}}{2R_C}$$

$$I_{CAC} = \frac{V_{CEQ}}{R_{AC}}$$

$$= \frac{V_{CC}}{2R_{AC}}$$

$$I = \frac{V}{R}$$

$$V_{CEA} = \frac{V_{CC}}{2}$$


$$I_C = \left(\frac{V_{CC}}{2R_C} + \frac{V_{CC}}{2R_{AC}} \right) \quad \text{--- toucher - y-axis}$$

I_{CMQ}


$(\frac{V_{CC}}{2R_C} + \frac{V_{CC}}{2R_{AC}})$

AC load line
DC load line

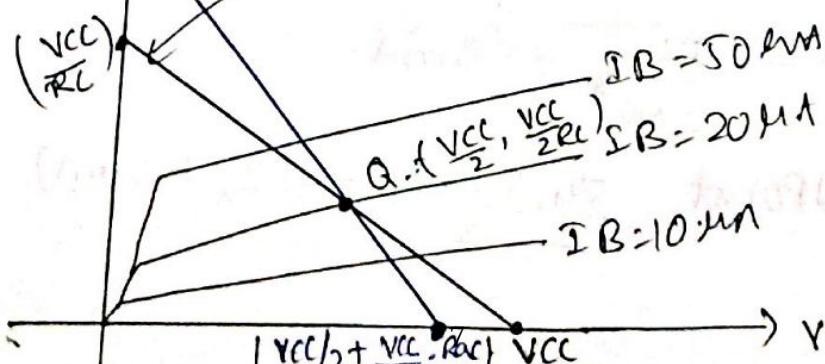
$$R_{AC} = \frac{R_C \cdot R_L}{R_C + R_L}$$



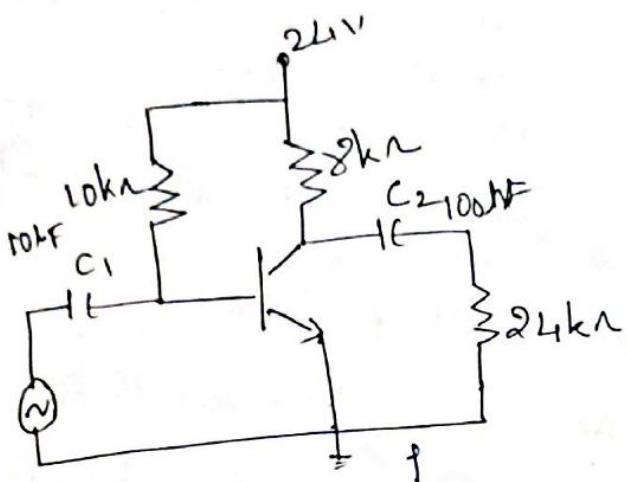For the following ckt transistor is an amplifier
shown in figure draw the DC load line, AC load line &
find Q point.




DC load line

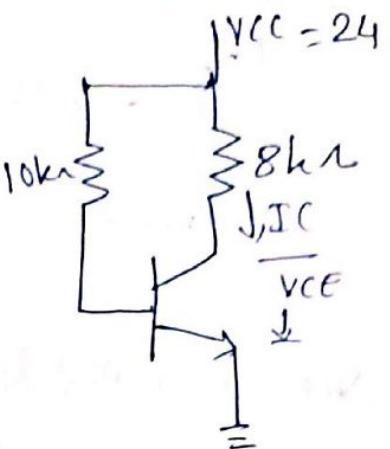

DC load line 1. AC Signal = 0 - 2. Apply only D.C. Capacitor opened -

3. actual characteristic

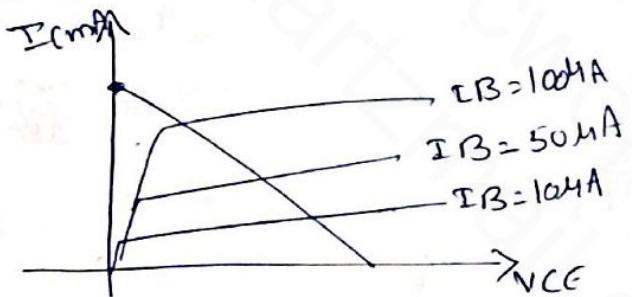

Apply KVL around acrom out loop.

$$24 = I_c \cdot 8k\Omega + V_{CE}$$


x-axis touches $I_c = 0$. $V_{CE} = 24V$

y-axis touches $V_{CE} = 0$

$$24 = I_c \cdot 8k\Omega + V_{CE} \Rightarrow 24 = I_c \cdot 8k\Omega + 0$$


$$I_c = \frac{24}{8 \times 10^3} = 3mA$$

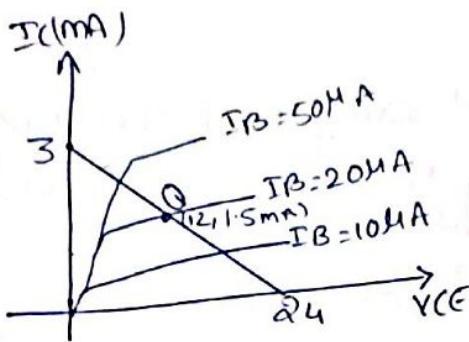Q point is midPoint $(\frac{24}{2}, \frac{3mA}{2}) = (12, 1.5mA)$



AC loadline:
Apply both AC and DC signals to draw the

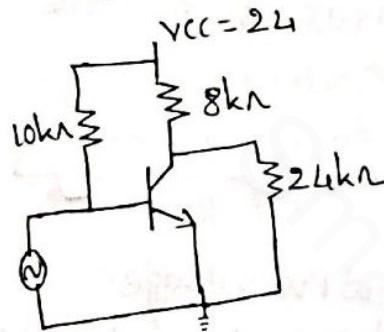AC loadline.
since AC in applied capacitor is short.




$$R_{ac} = R_L // R_C = \frac{8 \times 24}{8 + 24} = 6 \text{k}\Omega$$

$$\begin{aligned} V_{CE} &= V_{CEQ} + I_{CQ} \cdot R_{ac} \\ &= 12 + (1.5) \times 6 \times 10^3 \\ V_{CE} &= 21 \text{V} \end{aligned}$$

$$I_C = I_{CQ} + \frac{V_{CEQ}}{R_{ac}} = 1.5 \text{mA} + \frac{24}{6 \text{k}\Omega}$$

$$I_C = 3.5 \text{mA}$$

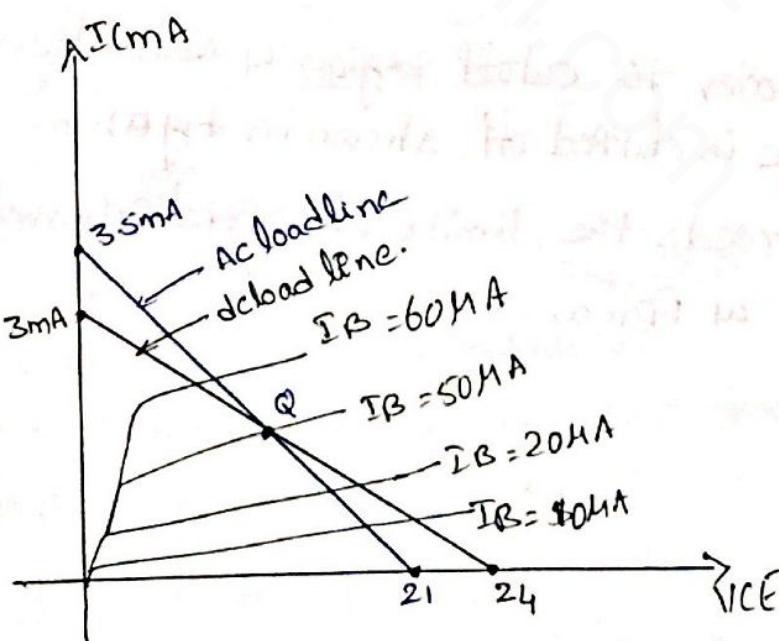

Need For Biasing:

Biasing: The process of choosing of proper supply voltages and resistors for obtaining the desired Q point is called biasing.

Need for biasing: The purpose of biasing circuit is to establish a proper stable dc operating point.

The Q point should be chosen such that


1. It should not exceed the limits of operation.
2. It should not nearer to saturation or cutoff regions.
3. It should be in active region - a midpoint for the dc load line.



Amplifier
symbol

fig (a)

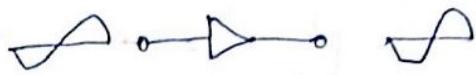Output voltage is clipped by
cutoff region



Output voltage
clipped by saturation

fig (b)

If a point is nearer to cutoff region or saturation region then output voltage is clipped off shown in fig (a), b.

It should not exceed the limits of operation such as the manufacturer's $P_{Dmax} \leq V_{CE} \cdot I_C$

Bias stability:

The Q point of a circuit is defined by specific values of the Q point of circuit has to maintained const.


Some problems of the

Some of the problems of maintaining the operating point stable.

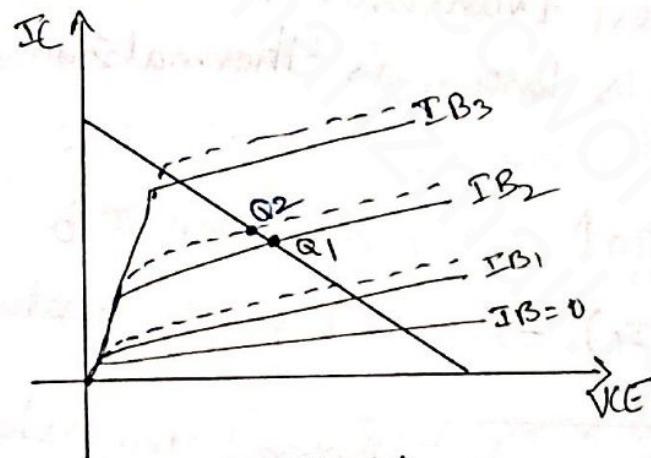- 1) If β value changes by changing of transistor.
- 2) Thermal instability.

If β value changes by changing of transistor.

Let us assume that the transistor is replaced by another of the same type. Then β value (hFE) changes since transistor is changed. If β changes I_C changes then Q point changes.



Q_1 — before tr. changed
 $Q_2 \rightarrow$ after tr. changed.

Thermal instability:

A second very important cause for bias instability is a variation in temperature.

As temperature changes I_{CO} changes. I_{CO} current doubles for 10°C temperature.


$$I_C = \beta I_B + (1+\beta) I_{CO}$$

As I_{CO} increases with temperature then I_C increases then Q point also changes.

If I_C increases Power dissipation increases www.inteworldupdates.org

$$P_D = V_{CE} \cdot I_C$$

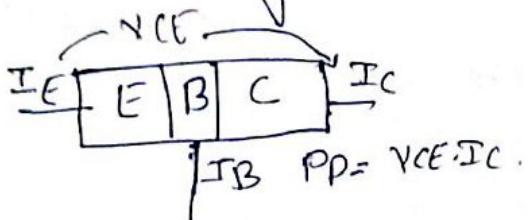If Power dissipation increases means that increasing of Power energy in terms of Heat.



If P_D increases Heat increases If Heat increases Temperature increases. If temperature increases I_{CO} increases If I_{IO} increases I_C increases this is a cumulative process at particular current of I_C .

If $P_D \gg P_{D\max}$ then transistor will be damaged this is known as thermal runaway or thermal instability.

Temperature $\uparrow \Rightarrow I_{CO} \uparrow \Rightarrow I_C = \beta I_B + (1+\beta) I_{IO}$

$I_C \uparrow \Rightarrow P_D \uparrow (P_D = V_{CE} \cdot I_C) \Rightarrow \text{Heat} \uparrow \Rightarrow \text{Temperature} \uparrow$

If $P_D \gg P_{D\max}$ transistor damaged. this is known as thermal runaway.

stabilization factors:

Biasing a transistor in the active region to maintain the operating point stable by keeping I_C, V_{CE} constant. The techniques normally used to do so may be classified in two categories

1> Stabilization techniques.

2> Compensation techniques.

Compensation technique:

Compensation technique refers to use of temperature (dependent) sensitive devices such as diodes, transistors, thermistors & resistors.

Stabilization techniques: (Biasing techniques)

Stabilization technique refers to use of temperature (independent) non-sensitive devices such as resistors.

The resistive biasing circuit which allows I_B to vary so as to keep I_C relatively constant with variations in I_{C0} , β & V_{BE} .

Stabilization factors

If temperature changes the I_C current changes due to three parameters.

1. I_{C0} :

For I_{C0} rise of temperature I_{C0} doubles. Then

I_C increases. since

$$I_C = \beta I_B + (1+\beta) I_{C0}$$

2. V_{BE}

If temperature increases of one degree centigrade then V_{BE} voltage decreases of 2.5mV.

$V_{BE} = -2.5 \text{ mV}/^\circ\text{C}$ If V_{BE} changes I_B changes

then I_C changes. (V_{BE} Voltage Forward bias voltage at JE.)

$$I_C = \beta I_B + (1+\beta) I_{C0} \Rightarrow I_C \propto \beta I_B$$

3. $\beta [hFE]$

If temperature increases I_{C0} increases I_C increases then β increases since $hFE = \beta = \frac{\Delta I_C}{\Delta I_B}$.

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

Since I_C increased β increases if β increases

$$\text{then } I_C = \beta \cdot I_B.$$

β value also changes w.r.t temperature.

since I_C dependent on three parameters I_{C0} , V_{BE} , β
there are three stabilization factors. S , S' , S''

stability factor S :

the extent to which the collector current I_C is stabilized with varying I_{C0} is measured by a stability factor S .

S can be defined as rate of change of collector current I_C with respect to collector leakage current I_{C0} by keeping both V_{BE} & β as constant.

$$S = \frac{dI_C}{dI_{C0}} \quad V_{BE}, \beta \text{ const}$$

as we know for CE Amplifier. at

$$I_C = \beta I_B + (1+\beta) I_{C0}. \quad \text{--- (1)}$$

$$S = \frac{dI_C}{dI_{C0}} \Rightarrow$$

differentiating the above equation with respect to I_C we get

$$1 = \beta \frac{dI_B}{dI_C} + (1+\beta) \frac{dI_{C0}}{dI_C}$$

$$1 - \beta \frac{dI_B}{dI_C} = (1+\beta) \frac{dI_{C0}}{dI_C}$$

$$1 - \beta \frac{dI_B}{dI_C} = \frac{1+\beta}{S}$$

$$S = \frac{(1+\beta)}{1 - \beta \frac{dI_B}{dI_C}}$$

$$S = \frac{(1+\beta)}{1-\beta \left(\frac{\partial I_B}{\partial I_C} \right)}$$

S should be small as possible to have better thermal stability.

stability factor S'

The stability factor S' is defined as the rate of change of I_C with V_{BE} keeping I_{CO} and β constant.

$$S' = \frac{\partial I_C}{\partial V_{BE}} \sim$$

$$S' = \frac{\partial I_C}{\partial V_{BE}} \quad I_{CO}, \beta \text{ const.}$$

stability factor S''


The stability factor S'' is defined as the rate of change of I_C w.r.t β keeping I_{CO} , V_{BE} const.

$$S'' = \frac{\partial I_C}{\partial \beta}$$

$$S'' = \frac{\partial I_C}{\partial \beta} \quad I_{CO}, V_{BE} \text{ const.}$$

stabilization techniques or Biasing techniques or methods of transistor biasing.

Fixed bias or Base Resistor method:

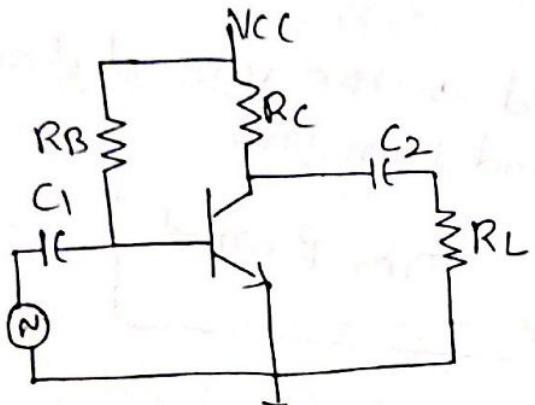

To measure the Q point we have to go for AC Analysis. For DC Analysis apply only DC voltage only.

Steps to find Q point :

1. AC (i/p signal) = zero.

2. Apply only DC signal.

$$\text{For DC } f=0 \quad X_C = Y_{2\pi f C} \quad X_C = \frac{1}{0} = \infty \quad |X_C = \infty|$$

3. capacitor opened.

4. Q (V_{CE} , I_C)

To find I_C :

a) apply KVL $\Sigma \omega$ across i/p loop find I_B (at base)

$$b) I_C = \beta I_B$$

To find V_{CE} :

apply KVL $\Sigma \omega$ across o/p loop (collector)

steps to find stability factor S

$$1. \text{ write the formula } S = \frac{1+\beta}{1-\beta \frac{dI_B}{dI_C}}$$


2. Apply KVL $\Sigma \omega$ to i/p mesh.

3. Substitute or Put $I_E = I_C + I_B$; simplify the expression.

4. Differentiate the equation by using I_B w.r.t I_C
so that $\frac{dI_B}{dI_C}$

5. Substitute $\frac{dI_B}{dI_C}$ in the $S = \frac{1+\beta}{1-\beta} \frac{dI_B}{dI_C}$

To find Q point.

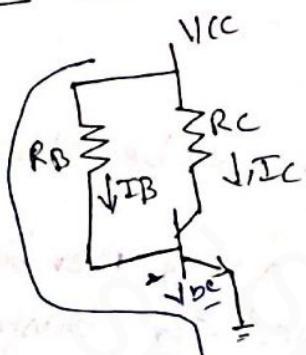

$$V_{CC} = I_B R_B$$

To find I_C
as apply KVL equation around i/p loop

$$V_{CC} = I_B R_B + V_{BE}$$

$$\begin{aligned} V_{BE} &= 0.7 \text{ Si} \\ &= 0.2 \text{ Ge.} \quad \text{y no neglect.} \end{aligned}$$

$$I_B = \frac{V_{CC}}{R_B}$$

b) $I_C = \beta I_B$


$$I_C = \beta \left(\frac{V_{CC}}{R_B} \right)$$

To find V_{CE}

Apply KVL eqn. around o/p loop (Collector)

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C$$

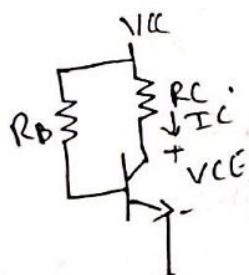

$$Q = (V_{CE}, I_C) = \left(V_{CC} - I_C R_C, \beta \left(\frac{V_{CC}}{R_B} \right) \right)$$

To find stability factors:

$$1. S = \frac{1+\beta}{1-\beta} \frac{dI_B}{dI_C}$$

2. Apply KVL eqn. to i/p loop.

$$V_{CC} = I_B R_B + V_{BE}$$

Differentiate w.r.t I_C

$$V_{CC} = I_B R_B + V_{BE}$$

$$0 = \frac{dI_B}{dI_C} R_B + I_O$$

$$\frac{dI_B}{dI_C} = 0$$

Substitute $\frac{dI_B}{dI_C} = 0$ in $S = \frac{1+\beta}{1-\beta \frac{dI_B}{dI_C}}$

$$S = \frac{1+\beta}{1-0} \Rightarrow S = 1+\beta$$

If S is smaller value of s , better will be the thermal stability, since β is a large quantity this is a very poor bias. ∴ in practice the circuit is not used for biasing the base.

To find S' steps

1. Apply KVL eqn. across i/p loop.

2. Put $I_E = I_C + I_B$.

3. Put $I_B = \frac{I_C - (1+\beta) I_O}{\beta} \quad \therefore I_C = \beta I_B + (1+\beta) I_O$

4. Differentiate I_C with respect to V_{BE} .


Apply KVL eqn. across i/p loop;

$$V_{CC} = I_B R_B + V_{BE}$$

$$\text{Put } I_E = I_C + I_B$$

$$3. \text{ Put } I_B = \frac{I_C - (1+\beta) I_O}{\beta}$$
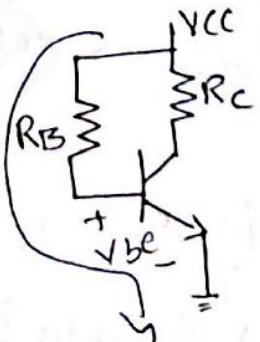
$$V_{CC} = \left(\frac{I_C - (1+\beta) I_O}{\beta} R_B + V_{BE} \right)$$



$$V_{CC} = \frac{I_C}{R_B} - \frac{(1+\beta)}{\beta} I_{IO} \cdot R_B + V_{be}$$

Differentiate above Eq. I_C w.r.t V_{be} .

$$0 = \frac{1}{\beta} R_B \cdot \frac{dI_C}{dV_{be}} - 0 + \frac{dV_{be}}{dV_{be}}$$

$$0 = \frac{R_B}{\beta} \frac{dI_C}{dV_{be}} + 1 \quad \frac{dI_C}{dV_{be}} = -\frac{1}{\frac{R_B}{\beta}} = -\frac{\beta}{R_B}$$

$$\boxed{s' = -\frac{\beta}{R_B}}$$

Relationship b/w s'

$$s = H\beta \\ s' = -\frac{\beta}{R_B} \quad \text{Add w sub 1}$$

$$s' = \frac{-\beta + 1 - 1}{R_B} = -\frac{(1+\beta) + 1}{R_B} = -\frac{s+1}{R_B}$$

$$s' = \frac{-s+1}{R_B}$$

To find s'' steps

1. Apply KVL equation across input loop.

$$2. \text{ Put } I_E = I_C + I_B$$

$$3. \text{ Put } I_B = \frac{I_C - (1+\beta)I_{IO}}{\beta}$$

4. find I_C in terms of voltage

5. Differentiate I_C w.r.t to β .

$$V_{CC} = I_B R_B + V_{be}$$


$$V_{CC} = \left(\frac{I_C - (1+\beta)I_{IO}}{\beta} \right) R_B + V_{be}$$

$$V_{CC} = \frac{I_C}{\beta} - \frac{(1+\beta)}{\beta} I_{IO} \cdot R_B + V_{be}$$

$$1+\beta = \beta$$

$$V_{CC} = \frac{I_C}{\beta} - I_{IO} \cdot R_B + V_{be}$$
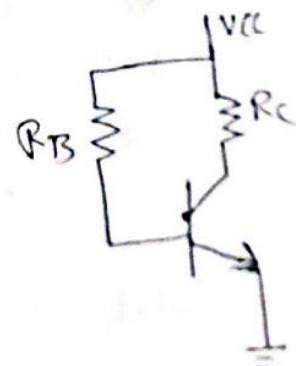
$$V_{CC} = \frac{I_C}{\beta} - V^1 + V_{be}$$



$$V_{CC} = \frac{I_C}{\beta} - V^I + V_{BE}$$

$$V_{CC} \cdot \beta + V^I \beta - V_{BE} \cdot \beta = I_C$$

$$I_C = \beta (V_{CC} + V^I - V_{BE}) \quad \text{--- (1)}$$

$$\frac{dI_C}{d\beta} = (V_{CC} + V^I - V_{BE}) (1)$$

$$\frac{dI_C}{d\beta} = V_{CC} + V^I - V_{BE}$$

From above eq. (1) $I_C = \beta (V_{CC} + V^I - V_{BE})$

$$\frac{dI_C}{d\beta} = \frac{I_C}{\beta}$$

$$S^{II} = \frac{I_C}{\beta}$$

$$S^{II} = \frac{I_C}{\beta}$$

$$S^{II} = \frac{I_C}{\beta}$$

Relationship b/w S^{II} & S

$$S = 1 + \beta$$

multiply & divide numerator & denominator by $1 + \beta$

$$1 + \beta$$

$$S^{II} = \frac{I_C(1 + \beta)}{\beta(1 + \beta)}$$

$$= \frac{S \cdot I_C}{\beta(1 + \beta)} = S'$$

~~Exhibit~~

→ smaller value of S better will be the thermal stability.


Minimum value of S is '1'

Maximum value of $S = 1 + \beta$


If for Ideal Amp, $S = 1$

If $S < 1 + \beta$ ckt is stable

$S = 1 + \beta$ ckt is unstable.

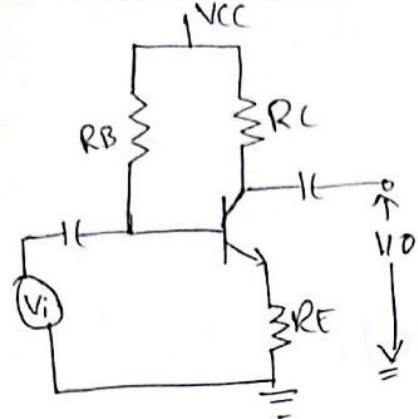Emitter - feedback bias

For Q Point by DC Analysis

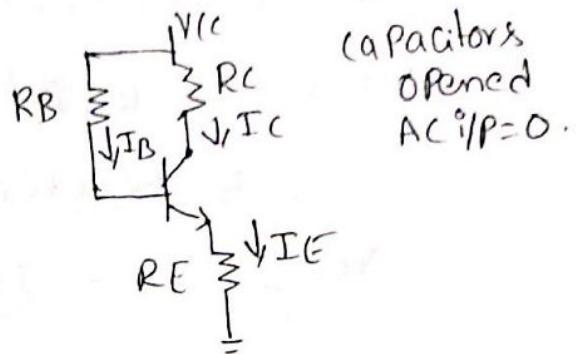

To find Qpoint :

To find I_C Apply KVL Eoo - acron o/p loop to find I_B

$$V_{CC} = I_B R_B + V_{BE} + I_E \cdot R_E \quad \therefore I_E = I_C + I_B$$

$$V_{CC} = I_B R_B + V_{BE} + (I_C + I_B) R_E$$

$$V_{CC} = I_B R_B + V_{BE} + I_C R_E + I_B R_E$$

$$I_C = \beta I_B$$

$$V_{CC} = I_B R_B + V_{BE} + \beta \cdot I_B R_E + I_B R_E$$

$$V_{CC} = I_B (R_B + \beta \cdot R_E + R_E) + 0.7 \quad \text{If } S_I = 0.7V \quad G_E = 0.2V$$

$$\frac{V_{CC}}{R_B + \beta R_E + R_E} = I_B$$

$$I_B = \frac{V_{CC}}{R_B + R_E (1 + \beta)}$$

$$I_C = \beta I_B$$

$$= \beta \left(\frac{V_{CC}}{R_B + R_E (1 + \beta)} \right)$$

To find V_{CE}

Apply KVL Eoo - acron o/p loop.

$$V_{CC} = I_C \cdot R_C + V_{CE} + I_E \cdot R_E$$

$$I_E = I_B + I_C$$

$$V_{CC} = I_C R_C + V_{CE} + I_B R_E + I_C R_E$$

$$V_{CC} = I_C R_C + V_{CE} + I_B R_E + I_C R_E$$

$$= I_C (R_C + R_E) + V_{CE} + I_B R_E$$

$$V_{CC} = \beta I_B (R_C + R_E) + V_{CE} + I_B R_E$$

$$= \beta I_B (\beta (R_C + R_E) + R_E) + V_{CE}$$

$$V_{CE} = V_{CC} - I_B (R_E(1+\beta) + \beta \cdot R_C).$$

$Q = (V_{CE}, I_C)$

$$Q = \left(V_{CC} - I_B (R_E(1+\beta) + \beta R_C), \frac{\beta \frac{V_{CC}}{R_B + R_E(1+\beta)}}{\beta + 1} \right)$$

To find S

$$\therefore S = \frac{1+\beta}{1-\beta \frac{\partial I_B}{\partial I_C}} \quad V_{BE}, \beta \text{ const.}$$

Apply KVL $\Sigma \epsilon = 0$ across i/p loop. 1 since I_B is there, we have to apply KVL $\Sigma \epsilon = 0$ across i/p loop

$$V_{CC} = I_B R_B + V_{BE} + I_E \cdot R_E$$

$$I_E = I_C + I_B.$$

$$V_{CC} = I_B R_B + V_{BE} + I_C \cdot R_E + I_B R_E$$

The $\Sigma \epsilon = 0$ should be in terms of I_B w/ I_C only.

Differentiate w.r.t I_C

$$0 = \frac{\partial I_B}{\partial I_C} R_B + 0 + \frac{\partial I_C}{\partial I_C} R_E + \frac{\partial I_B}{\partial I_C} R_E$$

$$0 = \frac{\partial I_B}{\partial I_C} (R_B + R_E) + \frac{\partial I_C}{\partial I_C} R_E$$

$$0 = \frac{\partial I_B}{\partial I_C} (R_B + R_E) + R_E$$

$$\frac{\partial I_B}{\partial I_C} = - \frac{R_E}{R_B + R_E}$$

$$s = \frac{(1+\beta)}{1-\beta(-RE/RB+RE)}$$

$$s = \frac{(1+\beta)}{1+\beta(RE/RB+RE)}$$

To find s'

$$s' = \frac{dI_C}{dV_{be}} \quad I_{C0}, \beta, \text{const.}$$

V_{be} voltage across i/p loop, no apply KVL equation across i/p loop.

$$V_{CC} = I_B R_B + V_{be} + I_E R_E$$

$$I_E = I_C + I_B$$

$$V_{CC} = I_B R_B + V_{be} + I_C \cdot R_E + I_B \cdot R_C$$

$$V_{CC} = I_B (R_B + R_E) + V_{be} + I_C \cdot R_E$$

$s' = dI_C/dV_{be} \rightarrow$ no in above equation I_C current only there I_{C0}, β . Should be there since I_{C0}, β are const.

$$I_C = I_B \beta + (1+\beta) I_{C0}$$

$$I_B = \frac{I_C - (1+\beta) I_{C0}}{\beta}$$

$$V_{CC} = \left[\frac{I_C - (1+\beta) I_{C0}}{\beta} (R_B + R_E) \right] + V_{be} + I_C \cdot R_E$$

$$V_{CC} = \frac{I_C}{\beta} (R_B + R_E) - \frac{(1+\beta) I_{C0} (R_B + R_E)}{\beta} + V_{be} + I_C \cdot R_E$$

Differentiate above eqn. I_C w.r.t. $V_{be} \Rightarrow I_{C0}$ w.r.t. β as const

$$0 = \left(\frac{R_B + R_E}{\beta} \right) \frac{dI_C}{dV_{be}} - \alpha + \frac{dV_{be}}{dV_{be}} + \frac{dI_C}{dV_{be}} R_E$$

$$0 = \frac{dI_C}{dV_{be}} \left(\left(\frac{R_B + R_E}{\beta} \right) + R_E \right) + 1$$

$$\frac{dI_C}{dV_{be}} = -1 / \left(\frac{(R_B + R_E)}{\beta} + R_E \right)$$

$$S' = -\frac{B}{(RB+RE)} + BRE$$

Relationship b/w S' & S

$$S = \frac{B}{1+B} \cdot \frac{RE}{RB+RE} \Rightarrow S = \frac{(1+B)RB+RE}{(RB+RE)+BRE}$$

$$S' = -\frac{B+1-1}{(RB+RE)+BRE} = -\frac{(1+B)+1}{(RB+RE)+BRE}$$

$$S' = -\frac{S}{(RB+RE)} + \frac{1}{(RB+RE)+BRE}$$

$$S_{\text{approx}}' = \frac{-S+1}{RB+RE}$$

To find S''

$$S'' = \frac{dI_C}{d\beta} \quad I_C, V_{BE} \text{ const.}$$

Apply KVL eqn. around top loop.

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$I_E = I_C + I_B$$


$$V_{CC} = I_B R_B + V_{BE} + I_C R_E + I_B R_E$$

$$V_{CC} = I_B (R_B + R_E) + V_{BE} + I_C R_E$$

$$I_B = \frac{I_C - (1+\beta)I_C}{\beta}$$

$$V_{CC} = \left(\frac{I_C - (1+\beta)I_C}{\beta} \right) (R_B + R_E) + V_{BE} + I_C R_E$$
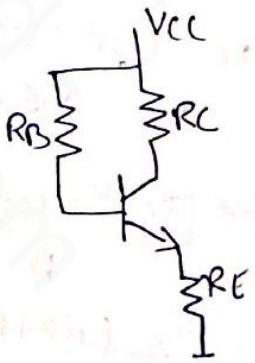
$$V_{CC} = \left(\frac{I_C}{\beta} - \frac{(1+\beta)I_C}{\beta} \right) (R_B + R_E) + V_{BE} + I_C R_E$$



$$V_{CC} = \frac{I_C}{\beta} (R_B + R_E) - \frac{(1+\beta)}{\beta} I_{IO} (R_B + R_E) + V_{BE} + I_C R_E$$

$$1+\beta \approx \beta$$

$$V_{CC} = \frac{I_C}{\beta} (R_B + R_E) - \frac{\beta}{\beta} I_{IO} (R_B + R_E) + V_{BE} + I_C R_E$$

$$V_{CC} = \frac{I_C}{\beta} (R_B + R_E) - I_{IO} (R_B + R_E) + V_{BE} + I_C R_E$$

$$I_{IO} (R_B + R_E) = V'$$

$$V_{CC} = \frac{I_C}{\beta} (R_B + R_E) - V' + V_{BE} + I_C R_E$$

$$V_{CC} = \frac{I_C}{\beta} (R_B + R_E) + I_C R_E - V' + V_{BE}$$

$$V_{CC} = I_C \left(\frac{R_B + R_E}{\beta} + R_E \right) - V' + V_{BE}$$

$$V_{CC} = I_C \left(\frac{R_B + R_E + \beta \cdot R_E}{\beta} \right) - V' + V_{BE}$$

$$I_C = \frac{V_{CC} + V' - V_{BE}}{\left(\frac{R_B + R_E + \beta \cdot R_E}{\beta} \right)} \quad \text{--- (1)} \quad \frac{d(u)}{v} = \frac{u' - u \cdot v'}{v^2}$$

$$I_C = (V_{CC} + V' - V_{BE}) \times \frac{\beta}{(R_B + R_E + \beta \cdot R_E)}$$

Differentiate above equation w.r.t β . I_{IO}, V_{BE} const

$$\frac{dI_C}{d\beta} = (V_{CC} + V' - V_{BE}) \left[\frac{R_B + R_E + \beta \cdot R_E (1) - \beta (0 + 0 + R_E (1))}{(R_B + R_E + \beta \cdot R_E)^2} \right]$$

$$\frac{dI_C}{d\beta} = (V_{CC} + V' - V_{BE}) \frac{R_B + R_E + \cancel{\beta \cdot R_E} - \cancel{\beta \cdot R_E}}{(R_B + R_E + \beta \cdot R_E)^2}$$

$$\frac{dI_C}{d\beta} = (V_{CC} + V' - V_{BE}) \cdot \frac{R_B + R_E}{(R_B + R_E + \beta \cdot R_E)^2}$$

From above Eq(1) I_C as

$$I_C = \frac{(V_{CC} + V^l - V_{BE})}{(R_B + R_E + R_{RE})} \cdot \beta.$$

$$S^{II} = \frac{(V_{CC} + V^l - V_{BE})}{(R_B + R_E + R_{RE})} \cdot \frac{(R_B + R_E)}{(R_B + R_E + R_{RE})}$$

$$= \left(\frac{I_C}{\beta} \right) \cdot \frac{R_B + R_E}{(R_B + R_E + R_{RE})}$$

$$S^{II} = \left(\frac{I_C}{\beta} \right) \frac{(R_B + R_E)}{R_B + R_E(1 + \beta)}$$

— ②

Relationship b/w SW S^{II}

$$S^{II} = \left(\frac{I_C}{\beta} \right) \frac{R_B + R_E}{R_B + R_E(1 + \beta)}$$

$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_B + R_E} \right)} = \frac{1 + \beta (R_B + R_E)}{R_B + R_E + \beta R_E} = \frac{(1 + \beta) (R_B + R_E)}{R_B + R_E (1 + \beta)}$$


$$\frac{R_E + R_E}{R_B + R_E (1 + \beta)} = \left(\frac{S}{1 + \beta} \right) — ③$$

S^{II} sub ③ in ②

$$S^{II} = \left(\frac{I_C}{\beta} \right) \left(\frac{S}{1 + \beta} \right)$$



$$S^{II} = \frac{S I_C}{\beta (1 + \beta)}$$

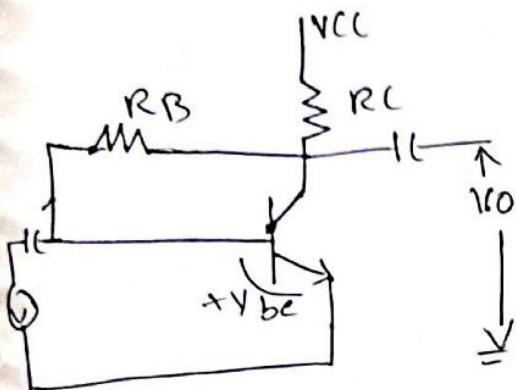Collector to Base Bias or
Collector Feedback bias.



For Q Point up for DC analysis
capacitors opened w.

$$AC^0/I_P = 0$$

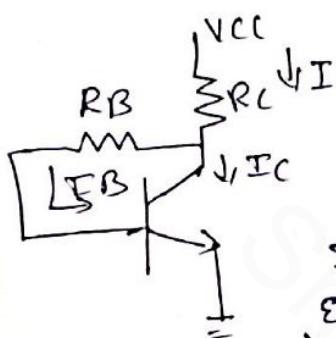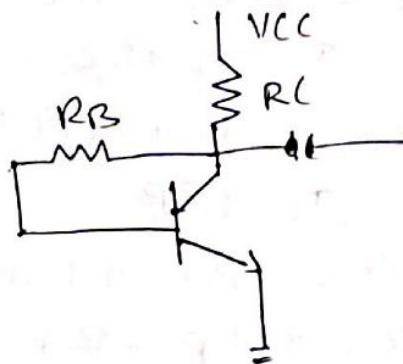

$I_C + I_B = I$.
If collector current I_C tends to increase due to either increase in temperature or transistor has been replaced by anyone higher value, the voltage drop across R_C increases and were V_{CE} to find Q Point. V_{FB} decreases which in turn compensates I_C .

To find I_B (I_f)

Apply KVL equation across I_f

$$V_{CC} = I_f \cdot R_C + I_B \cdot R_B$$

$$I_f = I_C + I_B$$

from collector I_B current is taken as feedback that's why cht is known as collector feedback bias.

$$V_{CC} = (I_C + I_B) R_C + I_B R_B$$


$$V_{CC} = I_C \cdot R_C + I_B \cdot R_C + I_B \cdot R_B$$

$$I_C = \beta I_B$$

$$V_{CC} = \beta I_B R_C + I_B R_C + I_B R_B$$

$$V_{CC} = I_B (R_C(1+\beta) + R_B)$$
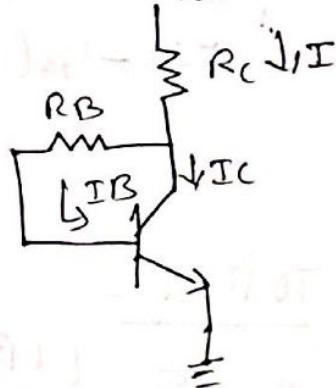
$$I_B = \frac{V_{CC}}{R_C(1+\beta) + R_B}$$



$$I_C = \beta I_B$$

$$I_C = \beta \times V_{CC} / R_C(1+\beta) + R_E$$

To find V_{CE}

Apply KVL equation across o/p loop;

$$V_{CC} = I \cdot R_C + V_{CE}$$

$$I = I_B + I_C$$

$$V_{CC} = I_B \cdot R_C + I_C \cdot R_C + V_{CE}$$

$$I_C = \beta I_B$$

$$V_{CC} = I_B \cdot R_C + \beta I_B \cdot R_C + V_{CE}$$

$$V_{CC} = I_B (R_C + \beta \cdot R_C) + V_{CE}$$

$$V_{CC} = I_B (R_C (1 + \beta)) + V_{CE}$$

$$V_{CE} = V_{CC} - I_B (R_C (1 + \beta)).$$

Q point (V_{CE} , I_C)

$$\left\{ V_{CC} - I_B (R_C (1 + \beta)), \frac{V_{CC} \cdot \beta}{R_C (1 + \beta) + R_E} \right\}.$$

To find S

$$\Delta S = \frac{1 + \beta}{1 - \beta} \frac{\partial \beta}{\partial I_C}$$


Apply KVL equation across i/p loop;

$$V_{CC} = I \cdot R_C + I_B R_B + V_{be}$$

$$I = I_B + I_C$$

$$V_{CC} = I_B R_C + I_C R_C + I_B R_B + V_{be}$$
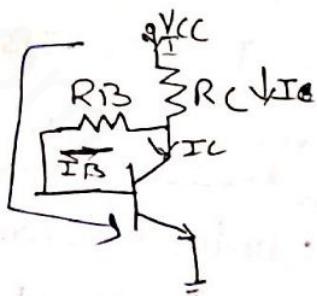
$$V_{CC} = I_B (R_C + R_B) + I_C R_C + V_{be}$$



Differentiate above w.r.t I_C

$$V_{CC} = I_B(R_C + R_B) + I_C R_C + V_{BE}$$

$$0 = \frac{dI_B}{dI_C} (R_C + R_B) + \frac{dI_C}{dI_C} R_C + 0.$$

$$= \frac{dI_B}{dI_C} (R_C + R_B) + (1) \cdot R_C.$$

$$\frac{dI_B}{dI_C} = -\frac{R_C}{R_C + R_B}.$$

$$S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)} = \frac{1 + \beta}{1 - \beta \left(-\frac{R_C}{R_C + R_B} \right)}$$

$$\boxed{S = \frac{1 + \beta}{1 + \beta \left(\frac{R_C}{R_C + R_B} \right)}} \\ = \frac{1 + \beta (R_C + R_B)}{R_C + R_B + \beta \cdot R_C} = \frac{(1 + \beta)(R_C + R_B)}{R_B + R_C(1 + \beta)}$$

$$S = \frac{(1 + \beta)(R_C + R_B)}{R_B + R_C(1 + \beta)}.$$

To find S'

$$S' = \frac{dI_C}{dV_{BE}}.$$

Apply KVL equation across input loop;

$$V_{CC} = I_R C + I_B R_B + V_{BE}$$

$$I = I_B + I_C$$

$$V_{CC} = I_B R_C + I_C R_C + I_B R_B + V_{BE}$$

$$V_{CC} = I_B (R_C + R_B) + I_C \cdot R_C + V_{BE}$$

$$I_B = \frac{I_C - (1 + \beta) I_O}{\beta}.$$

$$V_{CC} = I_B(R_C + R_B) + I_C R_C + V_{BE}$$

$$I_B = \frac{I_C - (1+\beta)I_{TO}}{\beta}$$

$$V_{CC} = \left(\frac{I_C - (1+\beta)I_{TO}}{\beta} \right) (R_C + R_B) + I_C R_C + V_{BE}$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B) - \left(\frac{1+\beta}{\beta} \right) I_{TO} (R_C + R_B) + I_C R_C + V_{BE}$$

Differentiate above equation I_C w.r.t V_{BE} & I_{TO} (out)

$$0 = \left(\frac{R_C + R_B}{\beta} \right) \frac{dI_C}{dV_{BE}} - 0 + \frac{dI_C}{dV_{BE}} R_C + \frac{dV_{BE}}{dV_{BE}}$$

$$= \left(\frac{R_C + R_B}{\beta} \right) \cdot \frac{dI_C}{dV_{BE}} + \frac{dI_C}{dV_{BE}} R_C + 1$$

$$\Rightarrow \frac{dI_C}{dV_{BE}} \left(\left(\frac{R_C + R_B}{\beta} \right) + R_C \right) = -1$$

$$\frac{dI_C}{dV_{BE}} = -1 / \left(\left(\frac{R_C + R_B}{\beta} \right) + R_C \right)$$

$$S' = -1 / \left(\frac{R_C + R_B}{\beta} + R_C \right)$$

Relationship b/w S & S'

$$S = \frac{1+\beta}{1-\beta \frac{dI_C}{dV_{BE}}} = \frac{1+\beta(R_C + R_B)}{R_B + R_C(1+\beta)} \approx \frac{\beta(R_C + R_B)}{R_B + R_C(1+\beta)}$$

$$S' = -\frac{\beta}{R_B + R_C(1+\beta)} = -\frac{S}{(R_C + R_B)}$$

$$S' = -\frac{S}{(R_C + R_B)}$$

To find S''

Apply KVL eqn. across i/p loop;

$$V_{CC} = I_B R_C + I_B R_B + V_{BE}$$

$$I = I_C + I_B$$

$$V_{CC} = I_C R_C + I_B R_B + V_{BE}$$

$$V_{CC} = I_C R_C + I_B R_B + I_B R_B + V_{BE}$$

$$I_B = \frac{I_C - (1+\beta)I_O}{\beta}$$

$$V_{CC} = I_B(R_C + R_B) + I_C R_C + V_{BE}$$

$$= \left(\frac{I_C - (1+\beta)I_O}{\beta} \right) (R_C + R_B) + I_C R_C + V_{BE}$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B) - \left(\frac{1+\beta}{\beta} \right) I_O (R_C + R_B) + I_C R_C + V_{BE}$$

$$\left(\frac{1+\beta}{\beta} \right) = 1 \dots \therefore H_B = \beta$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B) - I_O (R_C + R_B) + I_C R_C + V_{BE}$$

$$I_O (R_C + R_B) = \checkmark$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B) - V' + I_C R_C + V_{BE}$$

$$V_{CC} = I_C \left(\frac{R_C + R_B + R_C}{\beta} \right) - V' + V_{BE}$$

$$I_C = \frac{V_{CC} + V' - V_{BE}}{R_C + R_B + \beta R_C} - \beta \frac{(V_{CC} + V' - V_{BE})}{R_B + R_C (1+\beta)}$$

$$I_C = \beta \left(\frac{V_{CC} + V' - V_{BE}}{R_B + R_C (1+\beta)} \right)$$

$$I_C = \frac{\beta(V_{CC} + V^I - V_{BE})}{(R_B + R_C(1+\beta))} = (V_{CC} + V^I - V_{BE}) \cdot \frac{\beta}{R_B + R_C(1+\beta)}$$

Differentiate above equation w.r.t to β w.r.t I_C w.r.t V_{BE}

$$\frac{dI_C}{\beta} = (V_{CC} + V^I - V_{BE}) \cdot \frac{(R_B + R_C(1+\beta))(1) - \beta(0 + R_C(1))}{(R_B + R_C(1+\beta))^2}$$

$$= (V_{CC} + V^I - V_{BE}) \cdot \frac{R_B + R_C(1+\beta) - \beta R_C}{(R_B + R_C(1+\beta))^2}$$

$$= (V_{CC} + V^I - V_{BE}) \cdot \frac{R_B + R_C + \beta R_C - \beta R_C}{[R_B + R_C(1+\beta)]^2}$$

$$= (V_{CC} + V^I - V_{BE}) \cdot \frac{R_B + R_C}{[R_B + R_C(1+\beta)]^2}$$

$$S^{II} = \frac{V_{CC} + V^I - V_{BE}}{R_B + R_C(1+\beta)} \cdot \frac{(R_B + R_C)}{R_B + R_C(1+\beta)}$$

~~Relation~~

$$S^{II} = \frac{I_C}{\beta} \cdot \frac{(R_C + R_B)}{R_B + R_C(1+\beta)}$$

$$S^{II} = \frac{I_C(R_C + R_B)}{\beta(R_B + R_C(1+\beta))}$$


Relation ship b/w S^{II}

$$S = \frac{(1+\beta)(R_C + R_B)}{R_B + R_C(1+\beta)} \Rightarrow \left(\frac{S}{1+\beta}\right) = \frac{R_C + R_B}{R_B + R_C(1+\beta)}$$

$$S^{II} = \left(\frac{I_C}{\beta}\right) \left(\frac{S}{1+\beta}\right)$$

Collector-Emitter Feedback Bias.

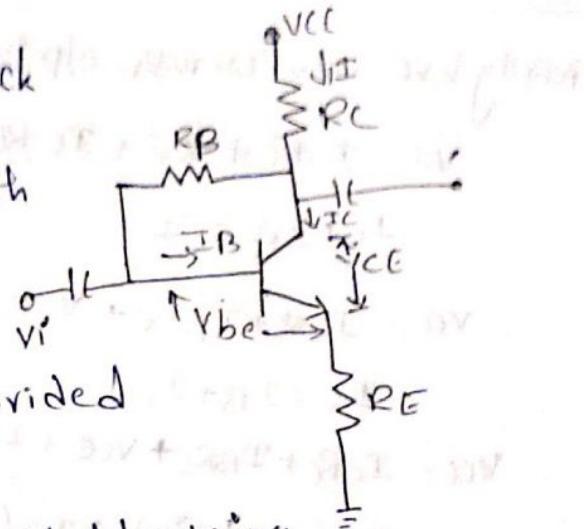The collector-emitter feedback bias circuit that can be obtained by applying both the collector-feedback or emitter feedback.



The collector feedback provided by using R_B .


The emitter feedback provided by using R_E .

Both feedbacks are used to control the collector current I_C w.r.t the base current I_B in opposite directions so stability factor is increased.

To find Q Point

To find I_B

Apply KVL law
across i/p loop.

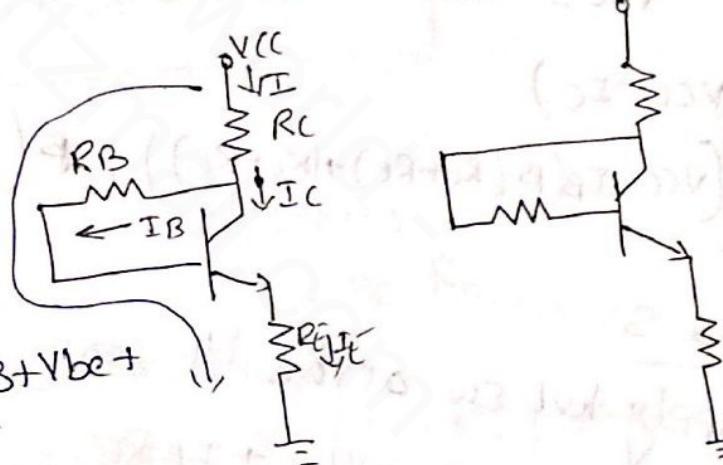

$$V_{CC} = I_B R_C + I_B R_B + V_{BE} + I_E R_E$$

$$I = I_B + I_C$$

$$I_E = I_B + I_C$$

$$\begin{aligned} V_{CC} &= I_B R_C + I_C R_C + I_B R_B + V_{BE} + I_B R_E + I_C R_E \\ &= I_B (R_C + R_B) + I_C (R_C + R_E) + V_{BE} \end{aligned}$$

$$I_C = \beta I_B$$

$$V_{CC} = I_B (R_C + R_B) + \beta I_B (R_C + R_E) + V_{BE}$$

$$V_{CC} = I_B ((R_C + R_B) + \beta (R_C + R_E)) + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{(R_C + R_B) + \beta (R_C + R_E)}$$

$$I_C = \beta I_B$$

To find V_{CE}

Apply KVL around 2nd loop;

$$V_{CC} = I \cdot R_C + V_{CE} + I_E \cdot R_E$$

$$I_C + I_B = I$$

$$V_{CC} = I_C R_C + I_B R_C + V_{CE} + I_E R_E$$

$$I_E = I_B + I_C$$

$$V_{CC} = I_C R_C + I_B R_C + V_{CE} + I_B \cdot R_E + I_C R_E$$

$$V_{CC} = I_C (R_C + R_E) + I_B (R_C + R_E) + V_{CE}$$

$$I_C = \beta I_B$$

$$V_{CC} = \beta I_B (R_C + R_E) + I_B (R_C + R_E) + V_{CE}$$

$$V_{CC} = I_B (\beta (R_C + R_E) + (R_C + R_E)) + V_{CE}$$

$$V_{CE} = V_{CC} - I_B (\beta (R_C + R_E) + (R_C + R_E))$$

$$Q = (V_{CE}, I_C)$$

$$= \left\{ \left(V_{CC} - I_B (\beta (R_C + R_E) + (R_C + R_E)), \beta \left(\frac{V_{CC} - V_{BE}}{(R_C + R_B) + \beta (R_C + R_E)} \right) \right) \right\}$$

To find S

Apply KVL around 1st loop;

$$V_{CC} = I_R C + I_B R_B + V_{BE} + I_E R_E$$


$$I = I_B + I_C$$

$$I_E = I_B + I_C$$

$$V_{CC} = I_B R_B + I_C (R_C + I_B R_B) + V_{BE} + I_B R_E + I_C R_E$$

$$V_{CC} = I_B (R_C + R_B) + I_C (R_C + R_E) + V_{BE}$$
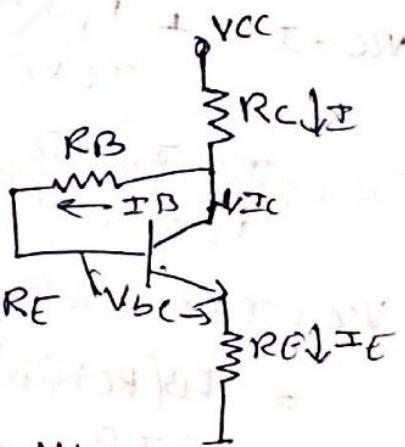
$$V_{CC} = I_B (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{BE}$$



$$V_{CC} = I_B (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{BE}$$

Differentiate above w.r.t. I_B .

$$0 = \frac{\partial I_B}{\partial I_C} (R_C + R_B + R_E) + \frac{\partial I_C}{\partial I_C} (R_C + R_E) + 0 \\ = \frac{\partial I_B}{\partial I_C} (R_C + R_B + R_E) + (R_C + R_E)$$

$$\frac{\partial I_B}{\partial I_C} = \frac{-(R_C + R_E)}{(R_C + R_B + R_E)}$$

$$S = \frac{1 + \beta}{1 - \beta} \left(\frac{-(R_C + R_E)}{(R_C + R_B + R_E)} \right) = \frac{1 + \beta}{1 + \beta} \frac{(R_C + R_E)}{R_C + R_B + R_E}$$

$$S = \frac{(1 + \beta)(R_C + R_B + R_E)}{(R_C + R_B + R_E) + \beta(R_C + R_E)}$$

To find S'

Apply KVL across i/p loop;

$$V_{CC} = I \cdot R_C + I_B R_B + V_{BE} + I_E \cdot R_E$$

$$I = I_B + I_C \quad I_E = I_B + I_C$$

$$V_{CC} = I_B (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{BE}$$

Differentiate above equation I_C w.r.t. V_{BE} . β, I_{IO} (cont)

$$So \quad I_B = \frac{I_C - (1 + \beta) I_{IO}}{\beta}$$

$$V_{CC} = \frac{I_C - (1 + \beta) I_{IO}}{\beta} (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{BE}$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B + R_E) - \frac{(1 + \beta)}{\beta} I_{IO} (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{BE}$$

Differentiate above eqn wrt V_{be}

$$0 = \left(\frac{R_C + R_B + R_E}{\beta} \right) \frac{dI_C}{dV_{be}} + 0 + \frac{dI_C}{dV_{be}} (R_C + R_E) + \frac{dV_{be}}{dV_{be}}$$

$$0 = \frac{dI_C}{dV_{be}} \left(\left(\frac{R_C + R_B + R_E}{\beta} \right) + (R_C + R_E) \right) + 1$$

$$\frac{dI_C}{dV_{be}} = - \frac{1}{\left(\frac{R_C + R_B + R_E}{\beta} \right) + (R_C + R_E)}$$

$$S' = - \frac{\beta}{(R_C + R_B + R_E) + \beta(R_C + R_E)}$$

$$S' = - \frac{\beta}{R_C(1+\beta) + R_E(1+\beta) + R_B}$$

$$S' = - \frac{\beta}{R_C(1+\beta) + R_E(1+\beta) + R_B}$$

To find S'

Apply KVL equation across i/p loop

$$V_{CC} = I \cdot R_C + I_B \cdot R_B + V_{be} + I_E \cdot R_E$$

$$I = I_B + I_C$$

$$I_E = I_B + I_C$$

$$V_{CC} = I_B (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{be}$$

$$I_B = \frac{I_C - (1+\beta)I_O}{\beta} \quad R_T = R_C + R_B + R_E$$

$$V_{CC} = \left(\frac{I_C - (1+\beta)I_O}{\beta} \right) R_T + I_C (R_C + R_E) + V_{be}$$

$$V_{CC} = \left(\frac{I_C - (1+\beta)I_O}{\beta} \right) (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{be}$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B + R_E) - \left(\frac{1+\beta}{\beta} \right) I_{C0} (R_C + R_B + R_E) + I_C (R_C + R_E) + V_{BE}$$

$$(1+\beta) \approx \beta.$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B + R_E) - I_{C0} (R_B + R_C + R_E) + I_C (R_C + R_E) + V_{BE}$$

$$I_{C0} (R_B + R_C + R_E) = V^1$$

$$S'' = \frac{\partial I_C}{\partial \beta}$$

$$V_{CC} = \frac{I_C}{\beta} (R_C + R_B + R_E) - V^1 + I_C (R_C + R_E) + V_{BE}$$

$$V_{CC} = I_C \left(\frac{R_C + R_B + R_E}{\beta} + (R_C + R_E) \right) + V_{BE} - V^1$$

$$V_{CC} = I_C \left(\frac{R_C + R_E + R_B + \beta(R_C + R_E)}{\beta} \right) + V_{BE} - V^1$$

$$I_C = (V_{CC} - V_{BE} + V^1) \times \frac{\beta}{(R_C + R_E + R_B) + \beta(R_C + R_E)}$$

$$\frac{\partial I_C}{\partial \beta} = (V_{CC} - V_{BE} + V^1) \cdot \frac{(R_C + R_E + R_B) + \beta(R_C + R_E) (1) - \beta(R_C + R_E)}{[(R_C + R_E + R_B) + \beta(R_C + R_E)]^2}$$

$$= (V_{CC} - V_{BE} + V^1) \frac{(R_C + R_E + R_B)}{[(R_C + R_E + R_B) + \beta(R_C + R_E)]^2}$$

$$= \frac{(V_{CC} - V_{BE} + V^1)}{(R_C + R_E + R_B) + \beta(R_C + R_E)} \times \frac{(R_C + R_E + R_B)}{[(R_C + R_E + R_B) + \beta(R_C + R_E)]}$$

$$= \frac{(V_{CC} - V_{BE} + V^1)}{(R_C + R_E + R_B) + \beta(R_C + R_E)} \times \frac{R_C + R_E + R_B}{(R_C + R_E + R_B) + \beta(R_C + R_E)}$$

from ①

$$S'' = \frac{I_C}{\beta} \cdot \frac{(R_C + R_E + R_B)}{(R_C + R_E + R_B) + \beta(R_C + R_E)}$$

$$S^{II} = \frac{I_C}{\beta} \left(\frac{R_C + R_E + R_B}{R_C + R_E + R_B + \beta(R_C + R_E)} \right)$$

Relationship b/w S^{II}

$$S = \frac{(1+\beta)(R_C + R_E + R_B)}{(R_C + R_E + R_B) + \beta(R_C + R_E)}$$

$$S^{II} = \frac{I_C}{\beta} \left(\frac{S}{1+\beta} \right)$$



voltage divider bias, self bias, or emitter bias.

The self bias also called as emitter bias or emitter resistor and potential divider circuit that can be used for low collector resistance as shown in fig.

The current in the emitter resistor R_E causes a voltage drop which is in the direction to reverse bias the emitter junction. For the transistor to remain in the active region, the base-emitter junction has to be forward biased. The required base bias is obtained from the power supply through the potential divider network of the resistors R_1 & R_L .

If I_C tends to increase say due to increase in T_0 with temperature, the current in R_E increases. Hence the voltage drop across R_E increases thereby decreasing the base current. As a result I_C is maintained almost constant.


dc analysis

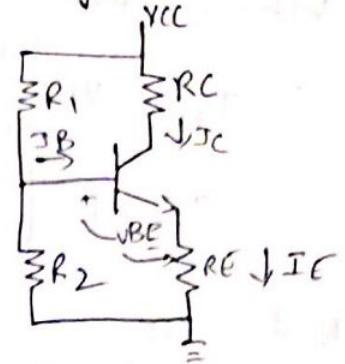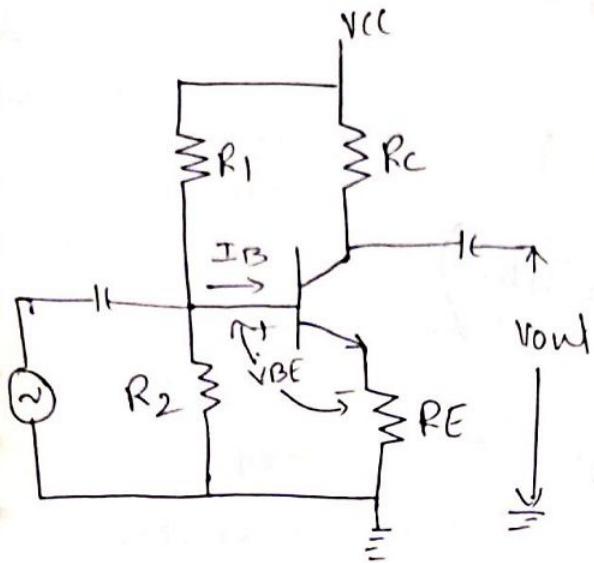

By applying Thvenins Theorem to the Circuit.

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$
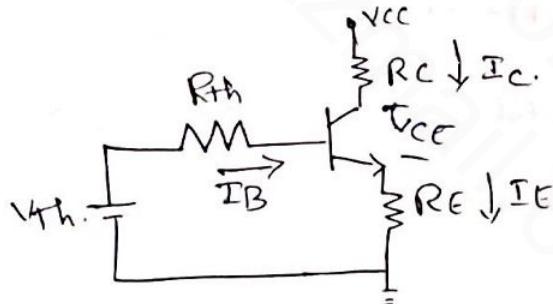
$$V_{Th} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$



$$V = IR$$

$$I = \frac{V_{CC}}{R_1}$$

$$V_{Th} = I \cdot R_{Th} \\ = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$V_{Th} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

find Q Point

$$V_{Th} = I_B \cdot R_{Th} + V_{be} + I_E \cdot R_E$$

$$I_E = I_C + I_B$$

$$V_{Th} = I_B \cdot R_{Th} + V_{be} + (I_C + I_B) \cdot R_E$$

$$V_{Th} = I_B \cdot R_{Th} + V_{be} + I_C \cdot R_E + I_B \cdot R_E$$

$$V_{Th} = I_B \cdot R_{Th} + V_{be} + I_C \cdot R_E + I_B \cdot R_E$$

$$I_C = \beta \cdot I_B$$

$$V_{Th} = I_B \cdot R_{Th} + V_{be} + \beta \cdot I_B \cdot R_E + I_B \cdot R_E$$

$$V_{TH} = I_B R_{TH} + V_{BE} + \beta I_B R_E + I_B R_E$$

$$V_{TH} = I_B (R_{TH} + \beta \cdot R_E + R_E)$$

$$I_B = V_{TH} / (R_{TH} + \beta \cdot R_E + R_E)$$

$$I_C = \beta \cdot \left(\frac{V_{TH}}{R_{TH} + R_E(1+\beta)} \right)$$

To find V_{CE}

Apply KVL Eqn. from o/p loop.

$$V_{CC} = I_C R_E + V_{CE} + I_E R_E$$

$$I_E = I_B + I_C$$

$$I_C = \beta I_B$$

~~$$V_{CC} = \beta I_B^2 + V_{CE} + I_B R_E + I_C R_E$$~~

~~$$= I_B (\beta R_E + R_E + R_E)$$~~

$$V_{CC} = I_C R_E + V_{CE} + I_E R_E$$

$$V_{CC} = I_C R_E + V_{CE} + I_B R_E + I_C R_E$$

$$= I_C (2R_E) + I_B R_E + V_{CE}$$

$$V_{CE} = V_{CC} - I_C (2R_E) + I_B R_E$$

To finds

$$S = \frac{1+\beta}{1-\beta \frac{\partial I_B}{\partial I_C}}$$

Apply V_{BE} across π P loop P.

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

$$I_E = I_C + I_B$$

$$V_{TH} = I_B R_{TH} + V_{BF} + (I_C + I_B) R_E$$

Differentiate above eqn w.r.t I_C

$$0 = \frac{\partial I_B}{\partial I_C} R_{TH} + 0 + R_E \left(\frac{\partial I_C}{\partial I_C} \right) + \frac{\partial I_B}{\partial I_C} R_E$$

$$\gamma = \frac{\partial I_B}{\partial I_C} \left(R_{TH} + R_E \right) + R_E$$

$$\frac{\partial I_B}{\partial I_C} = \left(-\frac{R_E}{R_{TH} + R_E} \right)$$

$$S = \frac{1+\beta}{1-\beta \left(-\frac{R_E}{R_{TH} + R_E} \right)}$$

$$S = \frac{1+\beta}{1+\beta \left(\frac{R_E}{R_{TH} + R_E} \right)}.$$

To find S'

$$S' = \frac{\partial I_C}{\partial V_{BE}}$$

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$


$$I_E = I_C + I_B$$

$$V_{TH} = I_B R_{TH} + V_{BE} + I_C R_E + I_B R_E$$

$$I_B = \frac{I_C - (1+\beta) I_{IO}}{\beta}$$

$$V_{TH} = \left(\frac{I_C - (1+\beta) I_{IO}}{\beta} \right) (R_{TH} + V_{BE} + I_C R_E)$$
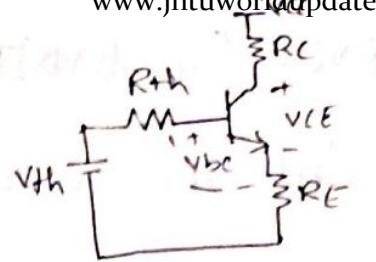
$$V_{TH} = \left(\frac{I_C - (1+\beta) I_{IO}}{\beta} \right) (R_{TH} + R_E) + V_{BE} + I_C R_E$$



$$\beta V_{th} = (I_C - (1+\beta)I_{(0)}(R_{th} + R_E)) + \beta V_{be} + \beta I_C \cdot R_t$$

diff. eqn. - I_C w.r.t V_{be} , $I_{(0)}$ & β as const

$$0 = \frac{dI_C}{dV_{be}} (R_{th} + R_E) + 0 + \beta \frac{dV_{be}}{dV_{be}} + \beta \cdot R_E \frac{dI_C}{dV_{be}}$$

$$= \frac{dI_C}{dV_{be}} (R_{th} + R_E) + \beta + \beta \cdot R_E \frac{dI_C}{dV_{be}}$$

$$0 \Rightarrow \frac{dI_C}{dV_{be}} (R_{th} + R_E + \beta R_E) + \beta$$

$$\frac{dI_C}{dV_{be}} = -\beta / (R_{th} + R_E + \beta R_E)$$

$$S' = -\beta / (R_{th} + R_E + \beta R_E)$$

$$S' = -\beta / (R_{th} + R_E (H_B))$$

Relationship S vs S'

$$S = 1 + \beta / 1 + \beta \left(\frac{R_E}{R_{th} + R_E} \right)$$

$$S = \frac{(1+\beta)(R_{th}+R_E)}{(R_{th}+R_E)+\beta R_E} = \frac{(1+\beta)(R_{th}+R_E)}{R_{th}+R_E(1+\beta)}$$

$$\frac{1}{R_{th}+R_E(H_B)} = S / (1+\beta)(R_{th}+R_E)$$

$$S' = -\beta / (R_{th} + R_E(1+\beta))$$

$$S' = (-\beta) \cdot \frac{S}{(1+\beta)(R_{th}+R_E)}$$

$$S' = -\frac{\beta S}{(1+\beta)(R_{th}+R_E)}$$

To find S^1 $\frac{dI_C}{d\beta}$ $I_{10}, V_{BE} \text{ const}$

APPLY KVL AROUND OIP LOOP:

$$V_{Th} = I_B R_{Th} + V_{BE} + I_E \cdot R_E$$

$$I_E = I_C + I_B$$

$$V_{Th} = I_B R_{Th} + V_{BE} + I_C R_E + I_B R_E$$

$$V_{Th} = I_B R_{Th} + V_{BE} + I_C R_E + I_B R_E$$

$$V_{Th} = I_B (R_{Th} + R_E) + V_{BE} + I_C R_E$$

$$I_B = \frac{I_C - (1+\beta) I_{10}}{\beta}$$

$$V_{Th} = \left(\frac{I_C - (1+\beta) I_{10}}{\beta} \right) (R_{Th} + R_E) + V_{BE} + I_C \cdot R_E$$

$$V_{Th} = \frac{I_C}{\beta} (R_{Th} + R_E) - \frac{(1+\beta) I_{10} (R_{Th} + R_E)}{\beta} + V_{BE} + I_C R_E$$

$$V_{Th} = I_C \left(\frac{R_{Th} + R_E + R_E}{\beta} \right) - \frac{(1+\beta) I_{10} (R_{Th} + R_E)}{\beta} + V_{BE}$$

$$V_{Th} = I_C \left(\frac{R_{Th} + R_E + \beta R_E}{\beta} \right) - \frac{(1+\beta) I_{10} (R_{Th} + R_E)}{\beta} + V_{BE}$$

$$(1+\beta) = \beta$$

$$V_{Th} = I_C \left[\frac{R_{Th} + R_E + \beta (R_E)}{\beta} \right] - I_{10} (R_{Th} + R_E) + V_{BE}$$

$$I_{10} (R_{Th} + R_E) = V^I$$

$$V_{Th} = I_C \left(\frac{R_{Th} + R_E (1+\beta)}{\beta} \right) - V^I + V_{BE}$$

$$\beta V_{Th} = I_C (R_{Th} + R_E (1+\beta)) - \beta V^I + \beta V_{BE}$$

$$I_C = \frac{V_{Th} - V_{BE} + V^I}{R_{Th} + R_E (1+\beta)} \times \beta$$

$$I_C = \frac{\beta(V_{Th} - V_{BE} + V)}{R_{Th} + RE(1+\beta)} = \frac{(V_{Th} + V - V_{BE})}{R_{Th} + RE(1+\beta)} \times \frac{\beta}{R_{Th} + RE(1+\beta)}$$

$$\frac{dI_C}{d\beta} = \frac{(V_{Th} + V - V_{BE}) \cdot [R_{Th} + RE(1+\beta)] - \beta[RE]}{[R_{Th} + RE(1+\beta)]^2}$$

$$\frac{dI_C}{d\beta} = (V_{Th} + V - V_{BE}) \cdot \frac{R_{Th} + RE(1) + \beta RE - \beta \cdot RE}{[R_{Th} + RE(1+\beta)]^2}$$

$$\frac{dI_C}{d\beta} = (V_{Th} + V - V_{BE}) \cdot \frac{R_{Th} + RE}{[R_{Th} + RE(1+\beta)]^2}$$

$$\frac{dI_C}{d\beta} = \frac{V_{Th} + V - V_{BE}}{R_{Th} + RE(1+\beta)} \times \frac{R_{Th} + RE}{R_{Th} + RE(1+\beta)}$$

$$S'' = \frac{I_C}{\beta} \frac{R_{Th} + RE}{R_{Th} + RE(1+\beta)}$$

Relationship b/w S & S''

$$S = 1 + \beta \left(\frac{RE}{1+\beta} \right) \left(\frac{R_{Th} + RE}{R_{Th} + RE} \right) = \frac{(1+\beta)(R_{Th} + RE)}{(R_{Th} + RE) + \beta RE}$$

$$S = \frac{(1+\beta)(R_{Th} + RE)}{R_{Th} + RE(1+\beta)}$$

$$\frac{R_{Th} + RE}{R_{Th} + RE(1+\beta)} = \frac{S}{1+\beta}$$

$$S'' = \frac{I_C}{\beta} \circ \frac{S}{1+\beta}$$

$$S'' = \frac{S \cdot I_C}{\beta(1+\beta)}$$

Bias compensation using diodes:

The Bias circuit are used to limit the variation in the operating collector current I_C caused by variations in I_{C0} , V_{BE} or B . The circuits are examples of feedback Amplifier. In Feedback Amplifier the gain is reduced drastically the amplification of signal.

Diode compensation

Diode compensation for V_{BE} (since I_C depends on V_{BE}) Diode compensation for I_{C0} .


Diode compensation for V_{BE} :

In fig(a) circuit utilizing the self bias stabilization technique with diode compensation. The diode is kept biased in the forward direction by the source V_{DD} and resistance R_d .

The diode is of same material as transistor.

So that the voltage V_o across the diode will have same temperature coefficient (-2.5 mV/C) as the Base to Emitter voltage, V_{BE} .

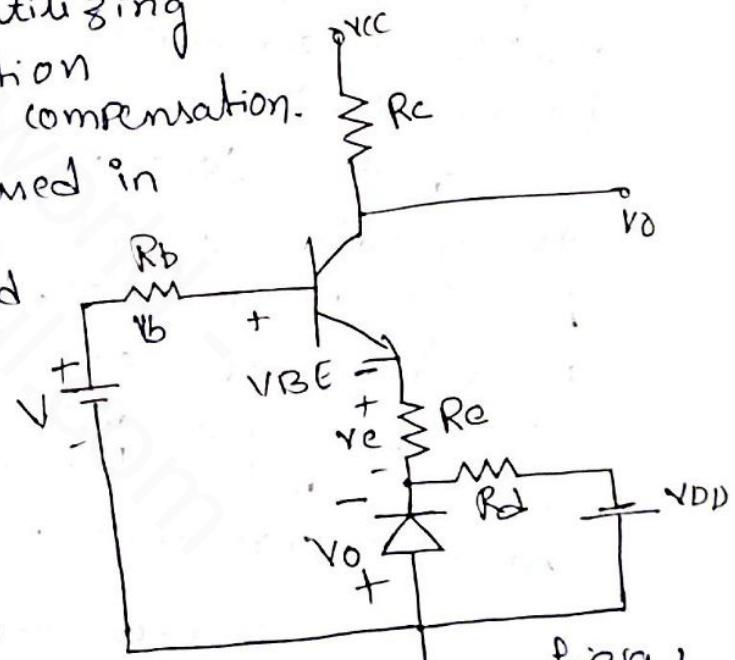$V_{BE} \approx V_o$ for temperature variations
i.e. -2.5 mV/C .



fig(a)

Apply KVL Eqn. across base then

$$V = V_B + V_{BE} + V_C - V_O$$

$$V = V_b + V_{BE} + V_C - V_0$$

$V_b = \text{const}$ V_b does not change with temp.

V_c does not change with temp.

$$V_C = \dots$$


V_{BE} & V_0 changes with temperature

(ie $-2.5mV/K$) & both are in opposite polarities so then the change in voltage due to temperature will be nullified.

Diode compensation for I_{CO} :

The stabilization against variations in I_{CO} , and is therefore useful for stabilizing germanium transistors.

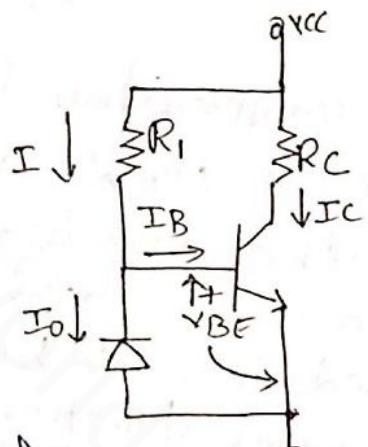If the diode & the transistor are of the same type and material, the reverse saturation current I_0 of the diode will increase with temperature at the same rate as the transistor collector reverse saturation current I_{CO} .



$$I = I_B + I_0 \quad \text{from figure} \quad \text{--- (1)}$$

$$I_C = \beta I_B + (1+\beta) I_{CO} \quad \text{--- (2)}$$

$$\text{from (1)} \quad I_B = I - I_0$$

Substitute in (2)

$$I_C = \beta I - \beta I_0 + (1+\beta) I_{CO}$$

$$I_C = \beta I - \beta I_0 + I_{CO} + \beta I_{CO}$$

$$(\beta+1) \approx \beta$$

$$I_C = \beta I_B - \beta I_{O2} + \beta I_{O1}$$

If doubley transistor are of same type of material then $I_O \approx I_{O1}$, then

$$I_C = \beta I_B$$

so that I_C remains constant even temperature changes.

Bias compensation using transistor.

If Q_1 & Q_2 are identical and have the same V_{BE} , their collector currents will be equal. hence $I_{C2} = I_{C1} = \text{const}$

$$I = I_{B1} + I_{B2} + I_{C1}$$


If temperature increases

The Q_1 transistor I_{C1} increases. I is a const current due to temperature. so that I_{B2} current decreases.

I_{B2} decreases then the current

$$\text{If } I_{B2} \text{ decreases } I_{C2} = \beta I_{B2} + (1+\beta) I_{O2}$$

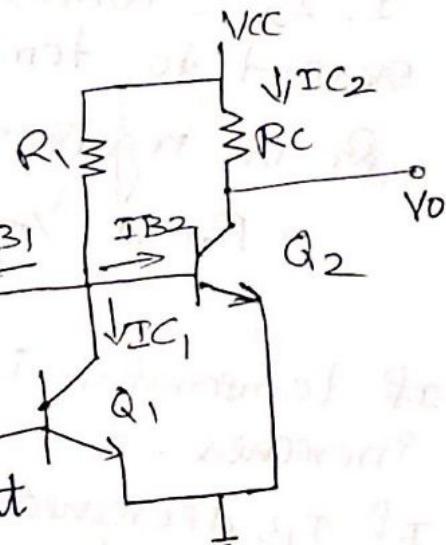tr. Q_2 decreases $\therefore I_{C2}$ current due to temperature increases then both are nullified. (since same amount of current I_{C1} changed due to temperature.)




Thermistor w/ sensistor compensation.

Thermistor R_T , having a negative temperature coefficient is connected in parallel to R_2

$$I = I_2 + I_T + I_B$$

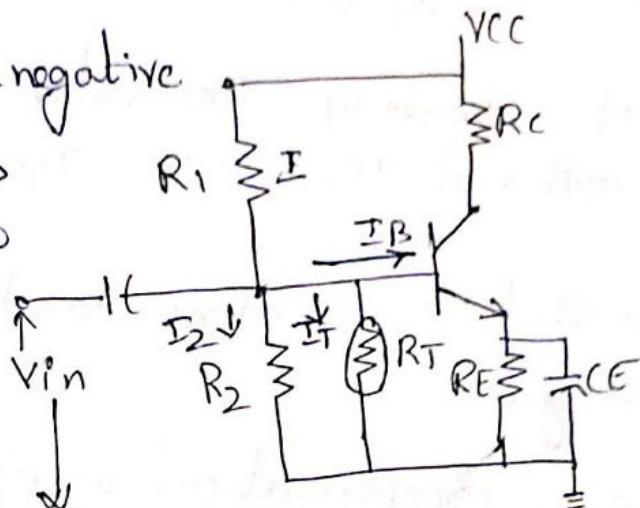I, I_2 = const; with respect to temperature.



R_T has negative temperature co. eff. if $R_T \propto 1/\text{Temp}$.

If Temp $\uparrow \Rightarrow R_T \downarrow$
Temp $\downarrow \Rightarrow R_T \uparrow$

If temperature increases R_T decreases then I_T increases. If I_T increases then I_B decreases. If I_B decreases by same amount of I_{IO} increased for transistor.


$$I_C = \beta I_B + (1+\beta) I_{CO} \\ = I_B \downarrow \propto I_{CO} \uparrow$$

So that I_C is maintained as constant.

Sensistor compensation.

Sensistor R_S , having a positive temperature is connected across R_1 .

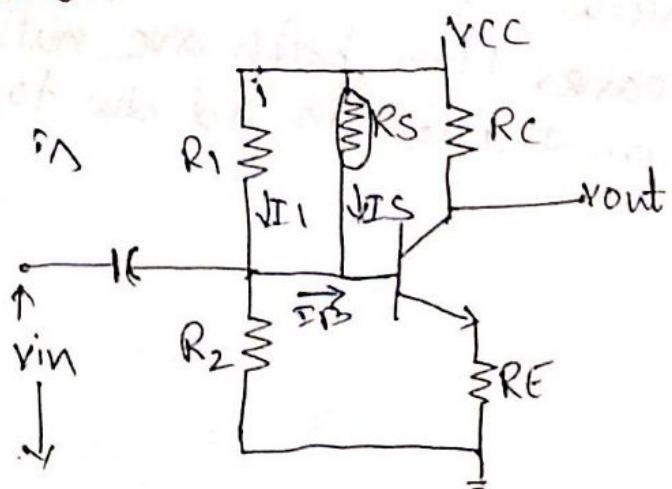i.e. Temp $\uparrow \Rightarrow R_S \uparrow$
Temp $\downarrow \Rightarrow R_S \downarrow$



$$I_B = I_1 + I_S.$$

If temperature increases I_{CO} increases by
R_S resistance increases

$$\text{Temp} \uparrow \Rightarrow R_S \uparrow \Rightarrow I_S \downarrow \Rightarrow I_B = I_1 + I_S$$

I_1 is const then I_B decreases.

$$T \uparrow \Rightarrow R_S \uparrow \Rightarrow I_S \downarrow \Rightarrow I_B \downarrow.$$

$$I_C = \beta I_B + \alpha(1+\beta) I_{CO}.$$

$$I_B \downarrow \quad \text{u} \quad I_{CO} \uparrow$$


so that the collector current I_C is
constant.

Tunnel diode:

If the concentration of impurity atoms is greatly increased, i.e 1 part in 10^3 . The device characteristics are completely changed. Then new diode was announced in 1958 Esaki. In P-n junction the concentration of impurity of about 1 part in 10^8 .

$w \propto \frac{1}{\sqrt{\text{Doping}}}$ So width of the depletion layer will be $\sqrt{\text{thin}}$.

Symbol:

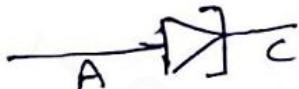Tunneling phenomenon:


$$w \propto \frac{1}{\sqrt{\text{doping}}}$$

The width of junction barrier varies inversely as the square root of impurity concentration. Since doping concentration is high, the width of the barrier and thickness of the barrier is $\frac{1}{50}$ of the wavelength of light. So that the charge carriers will be penetrating through the depletion layer almost at the speed of light, or if there a tunnel (a passage or way) in the tunnel diode and this quantum behaviour of the charge carriers is called tunneling phenomenon.


Material used:

- In Tunnel diode, the popularly used material is gallium Arsenide.
2. we can use Ge also but not preferable
 3. In Tunnel diode (fabrication) we never use silicon.

structure of heavily doped device:

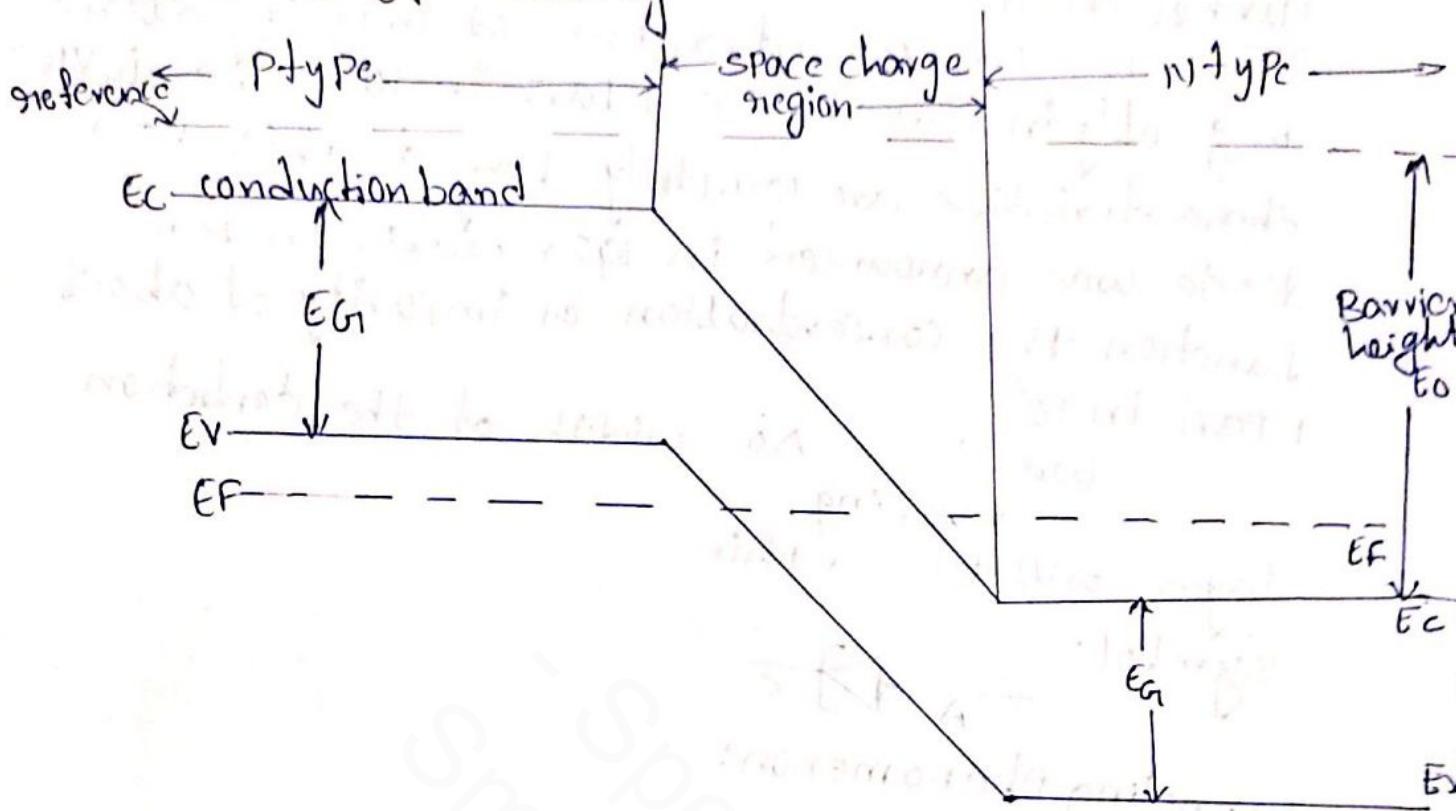

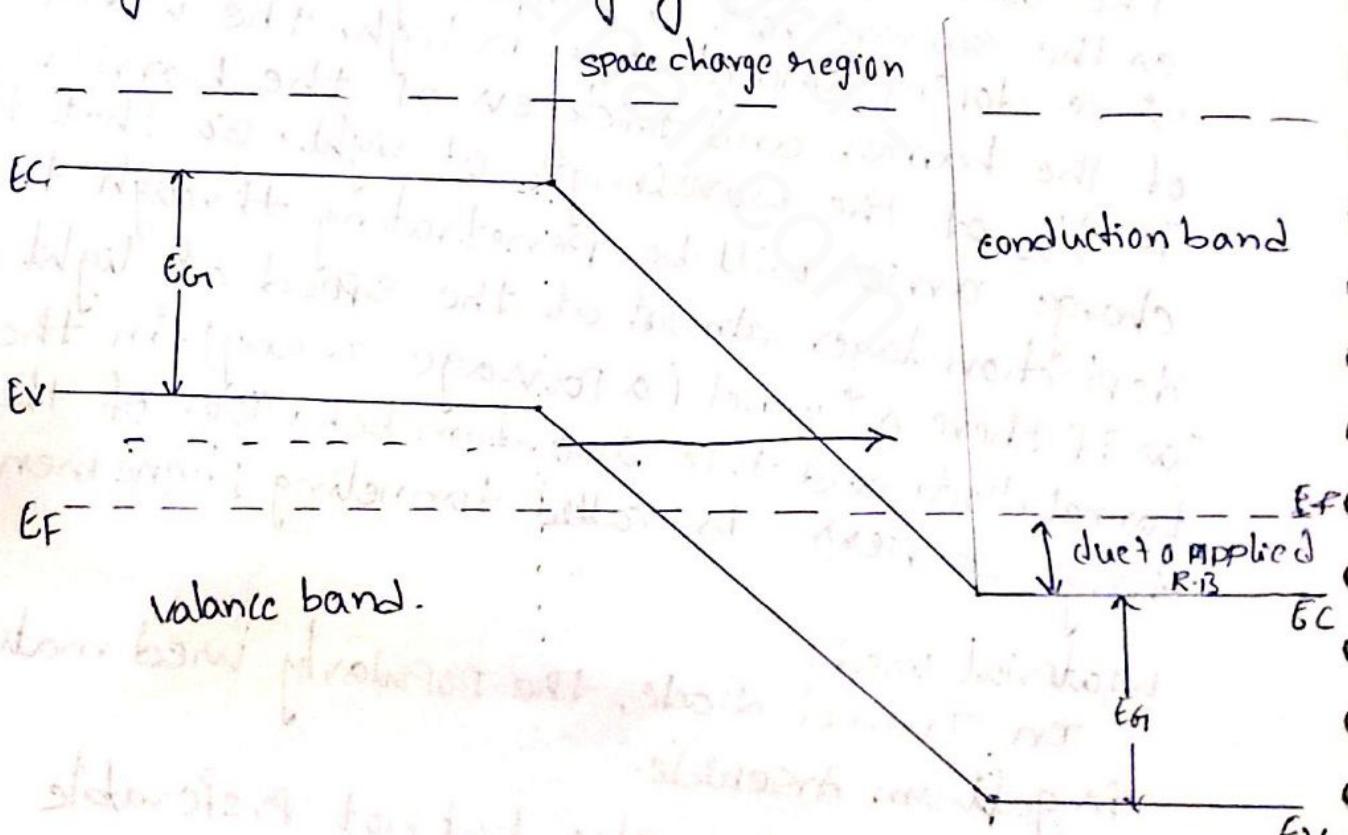fig④ open ckt for highly doped p-n diode.



fig⑤ when Reverse bias for highly doped diode.

Openckt :

For lightly doped p-n diode the fermi-level, the Fermilevel EF lies inside the forbidden Energy gap ie E_{G1} .

$$\text{As we know } EF = E_C - kT \ln\left(\frac{N_C}{N_D}\right) - \text{ for n type.}$$

For lightly doped diode semiconductor $N_D < N_C$ so that $\left(\frac{N_C}{N_D}\right)$ is positive number. So $EF < E_C$ and the Fermilevel lies inside the forbidden band.

For heavily doped diodes $N_D > N_C$ so $\frac{N_C}{N_D}$ is negative. So $(-kT \ln\left(\frac{N_C}{N_D}\right))$ becomes +ve w get added with E_C so then $EF > E_C$. So the Fermilevel of EF (n type material lies in the conduction band) similarly the $EF > E_V$ so the Fermilevel of EF for p type material lies in the valance band. ($\therefore N_A > N_V$) as shown in fig a.


$$E_{G1} = kT \ln\left(\frac{N_C \cdot N_V}{n_i^2}\right) - ①$$

$$E_0 = kT \left(\ln \frac{N_C \cdot N_V}{n_i^2} - \ln \frac{N_C}{N_D} - \ln \frac{N_V}{N_A} \right) - ②$$

from equations ① w ② from above discussion we can say that $E_0 > E_{G1}$ i.e. that the contact difference of potential energy E_0 now exceeds the forbidden energy gap E_{G1} . Hence the Picture of open ckt for highly doped diode.

In fig@ there are no filled states on one side of the junction w in fig(a) the Energy levels of Fermilevel is same on inside a p side. So no charge will flow in either direction, so no current.

Volt-Ampere characteristic of a diode.

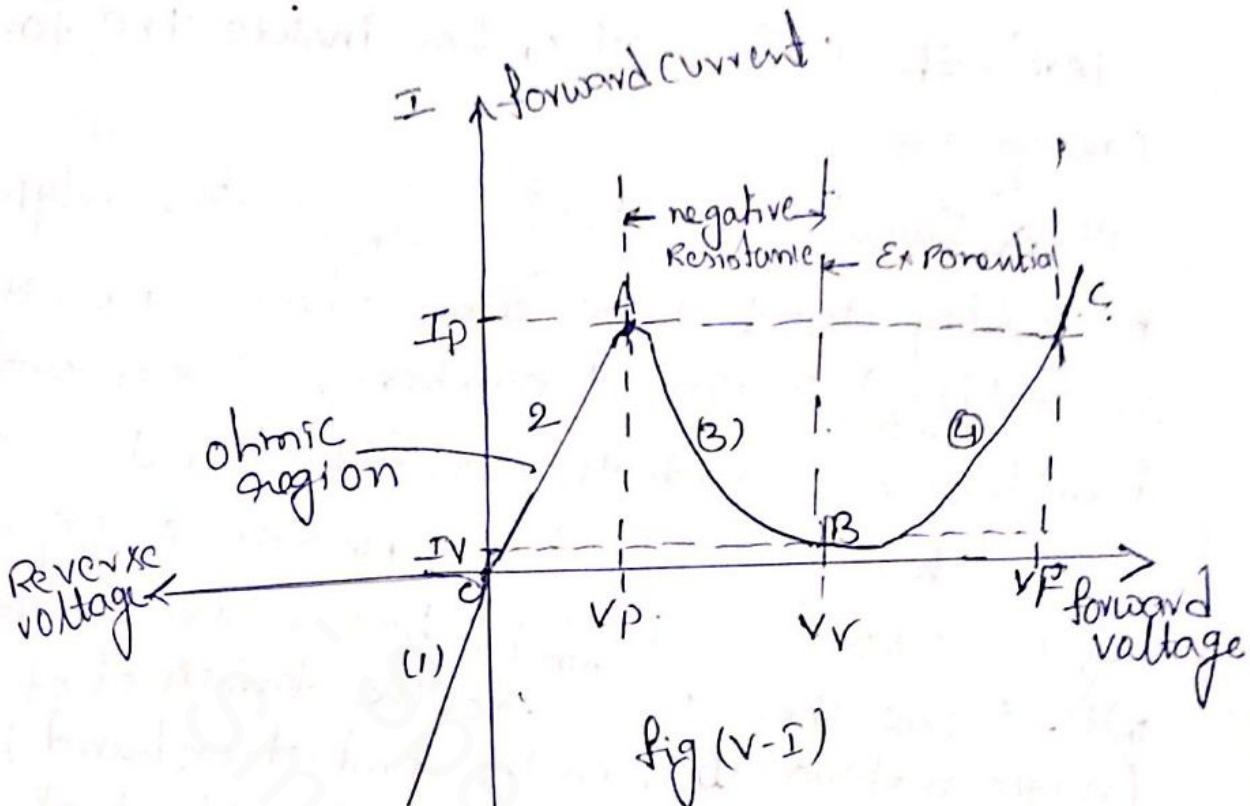

I_P = Peak current corresponding voltage.

V_V = Valley voltage.


V_F = Peak forward voltage

Reverse bias

Let if reverse bias voltage applied, the height of the barrier increased. When compared to the open circuit. When the diode is reverse biased the length of depletion layer will be increased.


Hence N side level must shift downward with respect to the P side level as shown in fig (b).

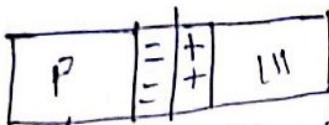In Fig(6) the energy levels of Fermi level is not same so the minority carrier tries to jump in to conduction band. for minority carriers barrier will not come in to picture since minority carriers and the barriers are not same charge of the opposite side junction. i.e. opposite charge of the opposite side junction.



↓ minority for P-side is electron.

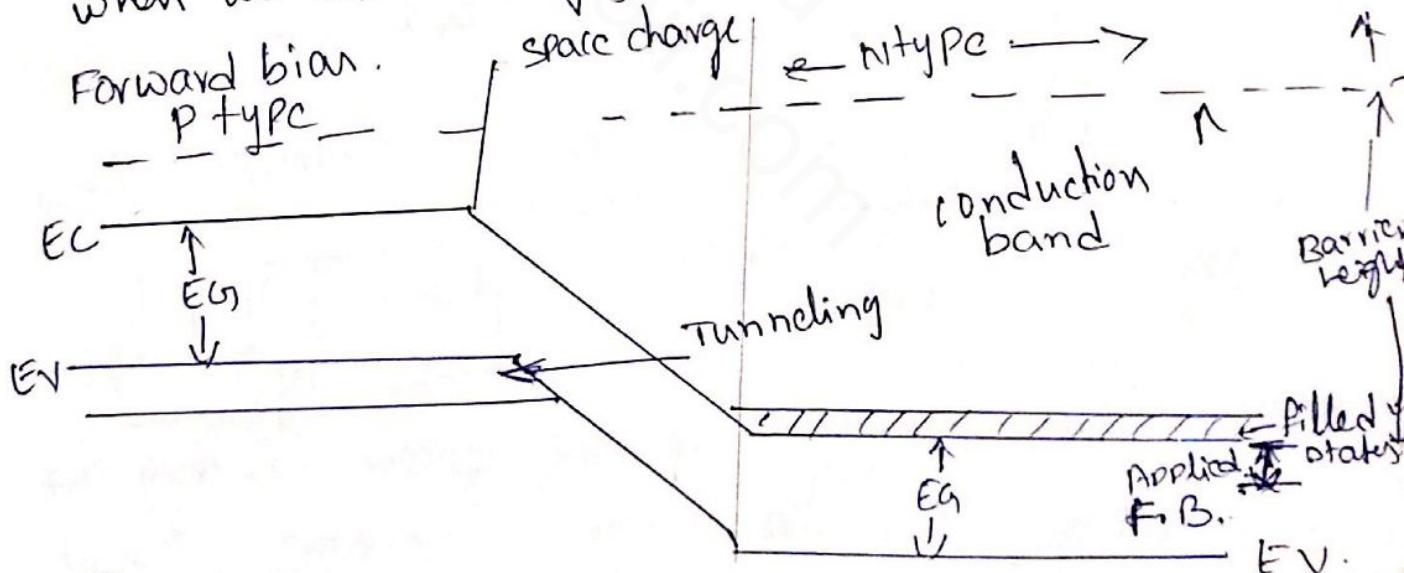Hence the electron minority will tunnel from P to the n-side giving side reverse diode current since it is heavily doped, if the increase of the reverse bias the electron (minority carriers) grows in size causing reverse current to increase as shown fig(V-I) graph for (i) in graph. whose Fermi level high that side electrons will increase when we applied energy



Fig(7)

consider for forward bias is applied to the diode so that the potential barrier decreased.

so for barrier height, hence n-side levels must shift upward with respect to P-side and Energy band picture is indicated as shown in fig fig(7)


photo Diode:

The interest in light sensitive devices has been increasing at an exceptional rate in recent years. The resulting field of opto electronics is receiving a great deal of research interest as efforts are made to improve efficiency levels. Light sources offers a unique source of energy. The energy transmitted as discrete packages called photons have a level directly related to the frequency of the travelling light wave.


$$W = hf \text{ Joules.} \quad h = \text{Planck's constant} \\ 6.624 \times 10^{-34} \text{ Joule sec}$$

$$\lambda = \frac{c}{f} \quad \lambda = \text{wavelength, meters} \\ c = \text{velocity of light } 3 \times 10^8 \text{ m/sec} \\ f = \text{frequency of the travelling wave hertz.}$$

$$A = 10^{-10} \text{ m.}$$

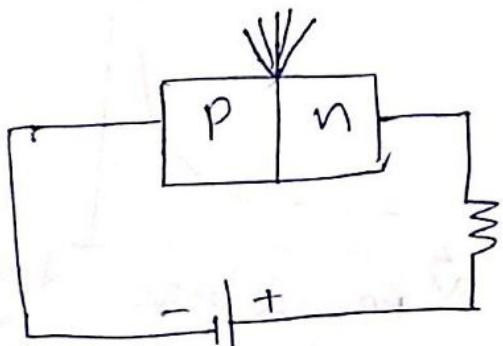



SCR silicon controlled rectifier.

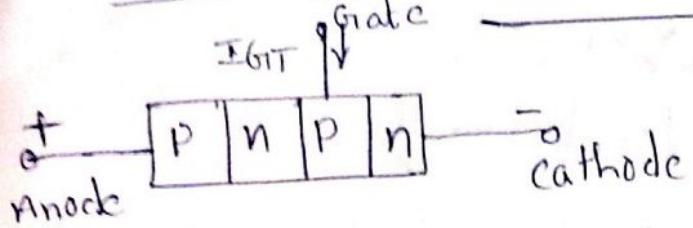

As terminology indicates the SCR is a rectifier constructed of silicon material with third terminal for control purpose. The basic operation of the SCR is different from that of the fundamental two layer semiconductor diode in that a third terminal, called a gate, determines when the rectifier switches from the open circuit to the short circuit state. It is not enough to simply forward bias the anode to cathode region of the device.

symbol

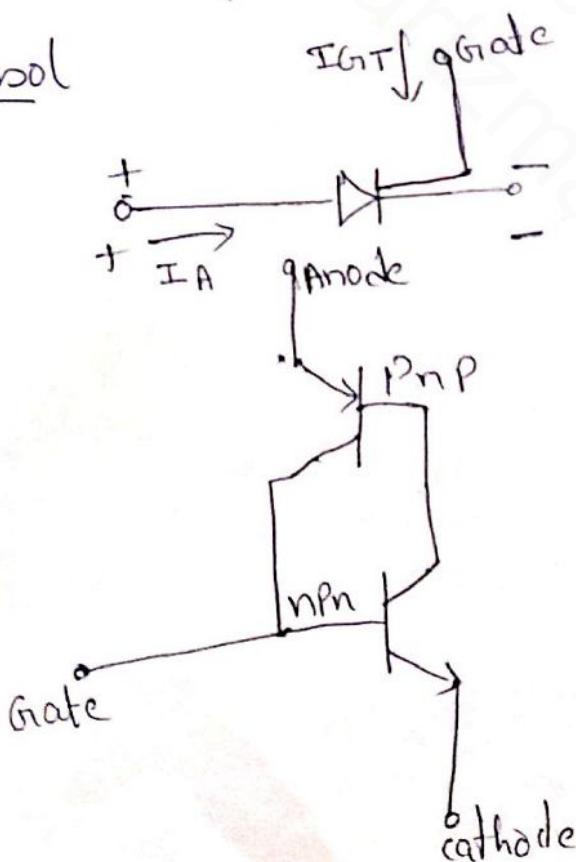

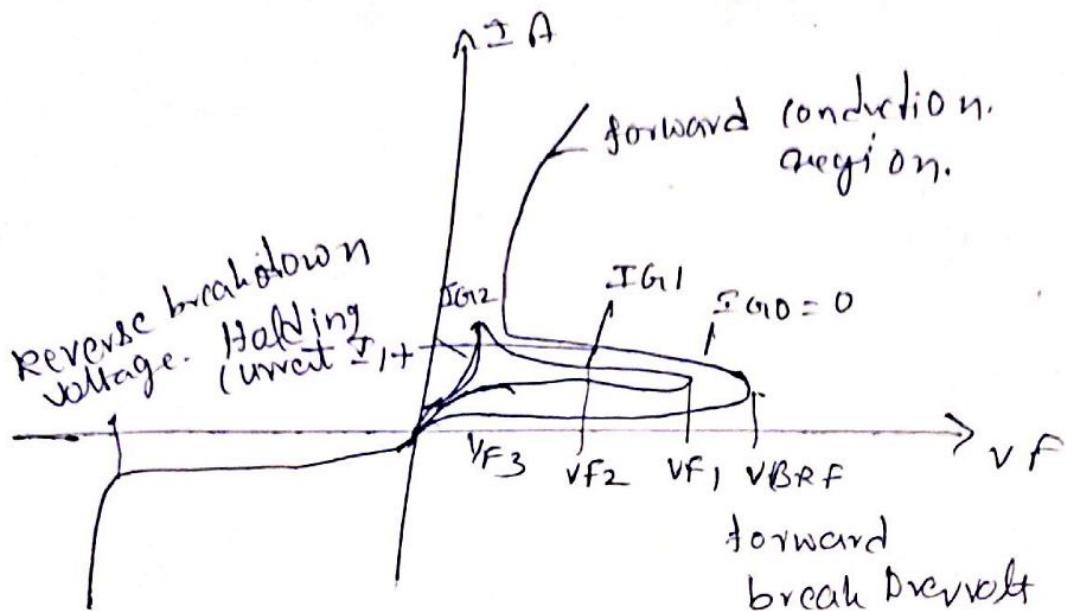

1. Forward breakdown voltage : V_{BRF} is the voltage which the SCR enters the conduction region.
2. Holding current : I_H is the value of current below which the SCR switches from conduction state to the forward blocking region under stated condition.
3. Forward & reverse blocking regions are the regions corresponding to the open circuit condition for the controlled switch.
4. Reverse breakdown voltage is equivalent to the zener or avalanche region of the fundamental two layer semiconductor diode.